

DN61

Dual cell powered ZXSC310 solution for a 1W high power white LED

Khagendra Thapa, Principal Systems Engineer, Zetex Semiconductors

Description

High power LEDs are increasingly being used in lighting applications (general illumination, portable, signage/security, traffic, automotive, architectural) as lumens, and efficacy of high power LEDs are increasing while the cost per lumens is decreasing.

Low cost, small and simple solutions are important in applications such as flashlight, signage and illuminations where 1W high power LED is powered from a low voltage supply as in single and dual cell batteries.

Figure 1 shows a typical simple low cost solution with a ZXSC310 driving a 1W LED with a typical forward voltage of 3.4V at 300mA from a dual cell battery. A dual cell supply will have a voltage range of 1.8V to 2.5V for NiCd and NiMH type batteries and up to 3V for alkaline type batteries. The component values are tabulated (see Tables 1 and 2), depending on the range of voltage which is defined by the battery chemistry.

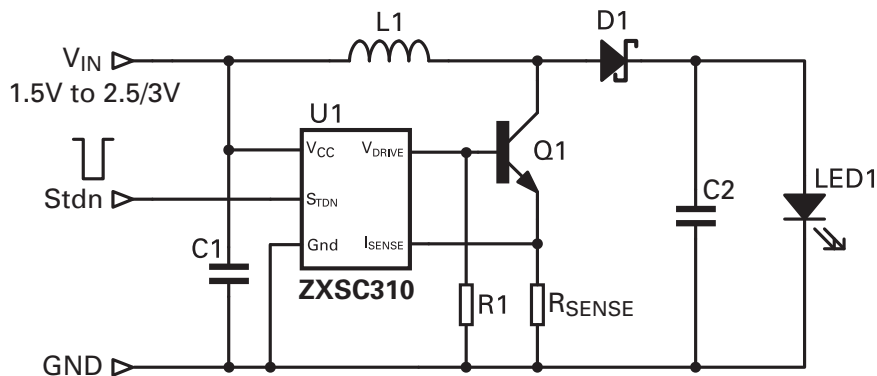


Figure 1 Typical dual cell battery powered 1W LED drive circuit

ZXSC310 is a constant current boost converter in a small SOT23-5 package. It has a typical drive current of 2.3mA at 1.8V. The drive current at 25°C is 1.5mA minimum at 1.5V supply.

The bipolar transistor switch, Q1, should have adequate voltage and peak switching current ratings, a very high transistor gain (h_{fe}), a very low saturation voltage (V_{CE}) and a small device package size with an adequate thermal capability. The transistor, Q1 in this application, is a low saturation voltage transistor, ZXTN25012EFL, with a very high gain of 700 at 1A collector current at 25°C to match the drive current from the Drive pin of the ZXSC310.

Note: If transistors with lower gain are used, then at lower temperatures, it may not support a full switching current and therefore proper operation may not start or may take few seconds to start.

The Schottky diode should have an adequate peak switching current rating and a very low forward voltage. The Zetex ZXSC1000 Schottky diode, SD1, has a low forward voltage. If operation at higher temperature is required then the low leakage, low forward voltage, Zetex ZLLS1000 can be used.

The choice of inductor, L1, depends on the desired switching frequency, the LED current, the input voltage, forward voltage of the Schottky diode, SD1, and the LED forward voltage.

Note: The LED current output is dependent on the input voltage, the LED forward voltage, the sense resistor and the inductor value.

DN61

Dual cell NiCd/NiMH battery solution

A dual cell NiCd/NiMH battery voltage range is 1.8V to 2.5V. Table 1 shows the component values for a dual cell NiCd/NiMH battery powered ZXSC310 solution for a 1W high power white LED. The efficiency and the LED current versus the input voltage performance are shown in Figures 2 and 3.

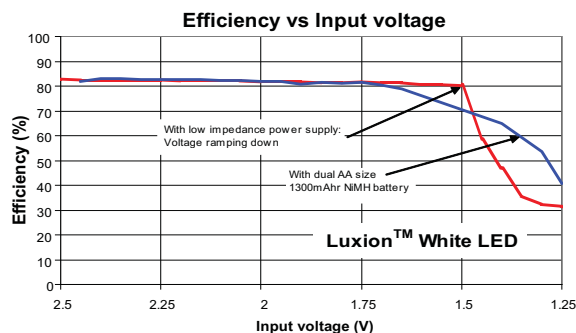


Figure 2 Efficiency vs. input supply voltage

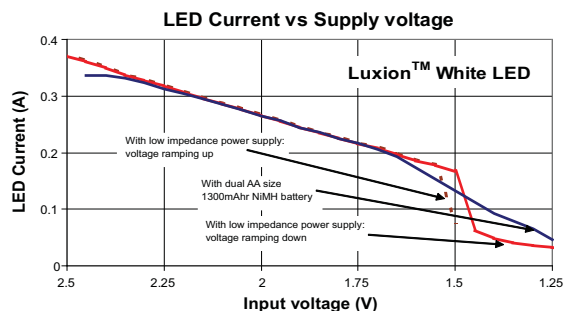


Figure 3 LED current vs. input supply voltage

Reference	Part no.	Value	Manufacturer	Contact details
U1	ZXSC310E5	LED driver	Zetex	www.zetex.com
Q1	ZXTN25012EFH	high gain, low $V_{CE(sat)}$	Zetex	www.zetex.com
SD1	ZHCS1000 or ZLLS1000	low forward voltage V_F	Zetex	www.zetex.com
L1	DO3316P-103	10 μ H, 2A	Coilcraft	www.coilcraft.com
R _{SENSE}	Generic	33m Ω	Generic	NA
R1	Generic	10k Ω	Generic	NA
C1	Generic	1 μ F, 6.3V, X7R	Generic	NA
C2	Generic	6.8 μ F, 6.3V	Generic	NA
LED1	LXHL-NW98	White LED; 3.4V	Lumileds	www.lumileds.com

Table 1 Bill of materials for dual cell NiCd/NiMH battery powered single 1W LED driver

Dual cell alkaline battery solution

The dual cell alkaline battery has a voltage range of up to 3V. Table 2 shows the component values for a dual cell alkaline battery powered ZXSC310 solution for a 1W high power white LED. The efficiency and the LED current versus the input voltage performance are shown in Figures 4 and 5.

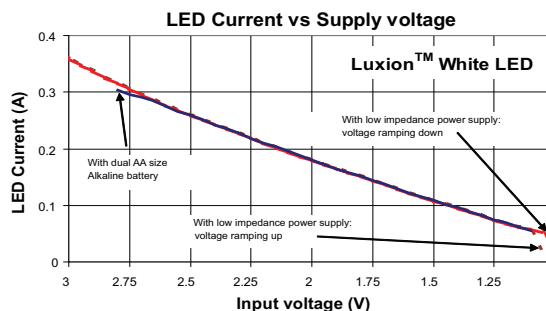
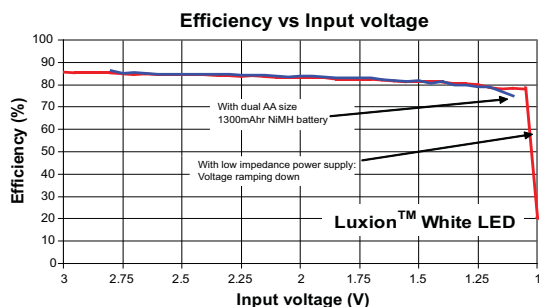


Figure 4 Efficiency vs. input signal voltage Figure 5 LED current vs. input supply voltage

Reference	Part no.	Value	Manufacturer	Contact details
U1	ZXSC310E5	LED driver	Zetex	www.zetex.com
Q1	ZXTN25012EFL	high gain, low $V_{CE(sat)}$	Zetex	www.zetex.com
SD1	ZHCS1000 or ZLLS1000	low forward voltage V_F	Zetex	www.zetex.com
L1	DO3316P-103	10uH, 2A	Coilcraft	www.coilcraft.com
R_{SENSE}	Generic	50m Ω	Generic	NA
R1	Generic	10k Ω	Generic	NA
C1	Generic	1 μ F, 6.3V, X7R	Generic	NA
C2	Generic	6.8 μ F, 6.3V	Generic	NA
LED1	LXHL-NW98	White LED	Lumileds	www.lumileds.com

Table 2 Bill of materials for dual cell alkaline battery powered 1W LED driver

Dimming and shutdown

In Figure 1, the shutdown pin, Stdn, can be tied to V_{CC} pin for normal operation. If the shutdown pin is taken to ground, the ZXSC310 enters standby mode with a low quiescent current of 5 μ A. The shutdown pin can also be used for PWM dimming by connecting a PWM signal. The LED current is then dependent on PWM duty ratio.

Thermal management

The LED junction temperature should be maintained within the specified maximum or derating curve, whichever is lower, by use of proper thermal management for lumens maintenance and LED protection. Size 0805 for the sense resistor is adequate.

DN61

Boot-strap operation

In boot-strap mode, the supply to the V_{CC} is from the output stage (cathode of SD1) to maintain the supply to the ZXSC310 at a reasonably constant voltage even when the battery voltage reduces. This improves the ZXSC310 drive pin current capability due to the reasonably constant voltage of 3.4V typical (or the forward voltage of the LED) at the V_{CC} pin, even though the battery voltage may drop below 1.5V.

The boot-strap allows the ZXSC310 to continue driving the LED even with battery supply drops below 0.8V after the initial successful start-up. The boot-strap mode is recommended for a single cell alkaline/NiMH/NiCd battery. The boot-strap mode can also be used in throw-away (single use) dual cell alkaline batteries to draw as much energy as possible before discarding the battery. Figures 6 and 7 show the efficiency and LED current versus battery voltage for a boot-strap mode of operation with an AA size dual cell alkaline battery.

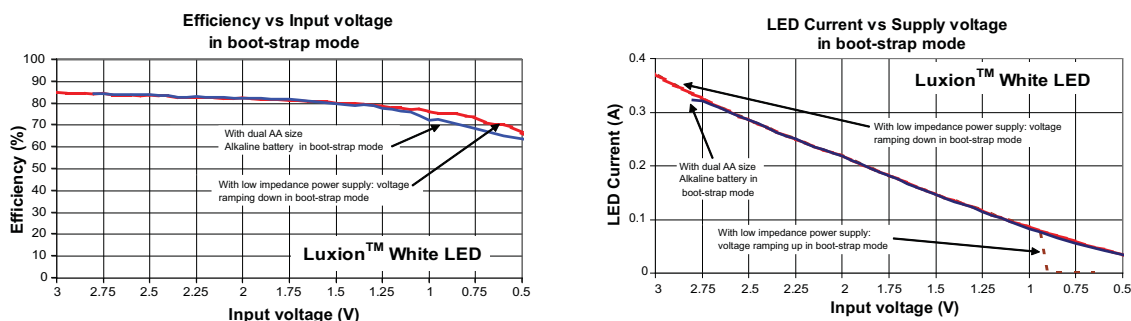


Figure 6 Efficiency vs. input supply voltage **Figure 7 LED current vs. input supply voltage**

Note: To prevent rechargeable batteries entering a deep discharge state, ZXSC310 devices can be shut down (by pulling the shutdown pin low to the ground) by an external circuit when the rechargeable battery voltage falls below its recommended minimum voltage. The boot-strap mode is not recommended with a ZXSC310 for dual/three cell NiCd/NiMH rechargeable batteries without a under voltage protection.

Intentionally left blank

DN61

Definitions

Product change

Zetex Semiconductors reserves the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Zetex with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Zetex does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

Life support

Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Zetex Semiconductors plc. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

Terms and Conditions

All products are sold subjects to Zetex' terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Zetex sales office .

Quality of product

Zetex is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Zetex Semiconductors or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: www.zetex.com/salesnetwork

Zetex Semiconductors does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

Green compliance

Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

Product status key:

"Preview"	Future device intended for production at some point. Samples may be available
"Active"	Product status recommended for new designs
"Last time buy (LTB)"	Device will be discontinued and last time buy period and delivery is in effect
"Not recommended for new designs"	Device is still in production to support existing designs and production
"Obsolete"	Production has been discontinued

Datasheet status key:

"Draft version"	This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.
"Provisional version"	This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice.
"Issue"	This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.

Zetex sales offices

Europe	Americas	Asia Pacific	Corporate Headquarters
Zetex GmbH Kustermann-park Balanstraße 59 D-81541 München Germany Telephone: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com	Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788 USA Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com	Zetex (Asia Ltd) 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com	Zetex Semiconductors plc Zetex Technology Park, Chadderton Oldham, OL9 9LL United Kingdom Telephone: (44) 161 622 4444 Fax: (44) 161 622 4446 hq@zetex.com

© 2007 Published by Zetex Semiconductors plc