

DN86

为多个1W LED组成的MR16代替灯减少零件数量、实现紧密的参考设计

Silvestro Russo, 2007 年 10 月

引言

MR16 灯属于多面向反射器灯的一种，通常以卤素灯丝囊作为光源。它们适用于很多零售和消费性应用，藉着独特的尺寸、可配置性、聚光能力和美观性，发挥实用性和创意。不过，低效率、热量产生和卤素囊处理问题往往成为了这种技术的缺点。MR16 灯一般采用 12V DC 或 12V AC 通用电磁式变压器下操作。

LED 是一个替代卤素灯的理想选择，因为它具有更高效能及无热辐射。

这款参考设计可以装设于 MR16 型 LED 射灯的标准连接器空间。它经过了优化，在零件数量以至热性能方面，都更臻完善。这款设计一般可在镜面部分配合 3 个 1W LED 使用，更可以作出调整，满足照明系统设计人员的要求。

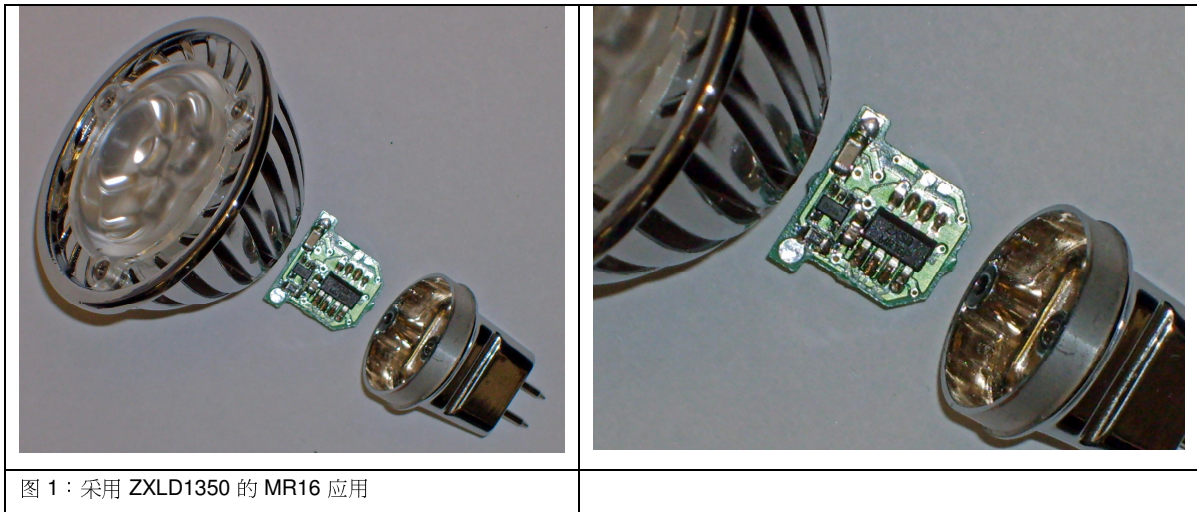


图 1：采用 ZXLD1350 的 MR16 应用

规格书

建议用户在使用此设计手册的同时，也参考 ZXLD1350 的规格书。请浏览：

<http://www.zetex.com/3.0/pdf/ZXLD1350.pdf>

描述

图 2 是利用 ZXLD1350 和 ZXSBMR16T8 实现的 MR16 灯解决方案的系统接线图，表 1 则提供了物料清单。

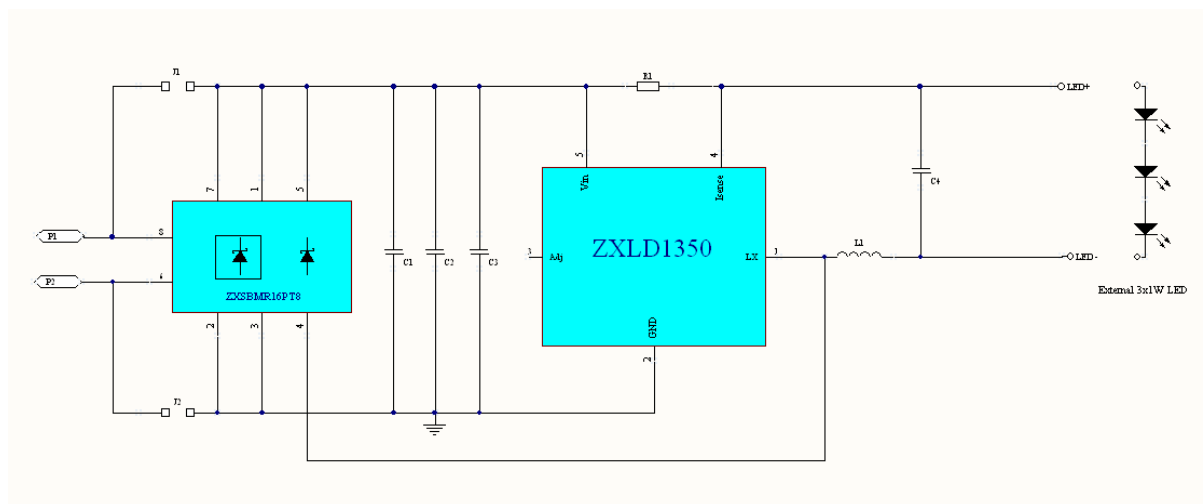


图 2 – ZXLD1350 MR16 灯解决方案的系统接线图

ZXLD1350 是为 350mA 或以下的 LED 电流驱动应用而设计。这款单片式 NMOSFET 大小适中，提供具有成本效益的芯片尺寸，额定电流为 400mA，在迟滞操作模式下 (电流波形从标称电流设定点约升降 +/-15%) 提供足够的裕度。ZXLD1350 的主要特点包括：

- 高至 380mA 的输出电流
- 宽阔的输入电压范围：7V 至 30V
- 内部 30V 400mA NDMOS 开关
- 高效率 (高于 90%)
- 高至 1MHz 的开关频率

ZXSBR16T8 是一款能够节省空间又具有热效率，并且特别为满足 MR16 应用的关键要求设计的器件。它包含一个全桥和一个空转二极管，以低泄漏的 1A、40V 肖特基二极管来实现标称 12V AC 输入操作。相比于采用一体式设计标准硅式二极管，这种肖特基桥与嵌入式续流二极管的组合有助于提升系统的效率。参考设计中具备旁路焊接点，可以省略桥式整流器，最终的电灯设计亦适用于纯 DC 操作。

由于 ZXLD1350 采用了迟滞式转换电路拓扑，因此转换效率取决于几项因素 – 输入电压、目标电流和 LED 数量。当中还设有以 Excel 为基础的计算器，用于系统的初始评测和决定零件选择。

详情可浏览 <http://www.zetex.com/3.0/otherdocs/zxld1350calc.xls>

系统效率和 LED 电流测量皆包含在设计中，ADJ 管脚保持浮动，以测量器件中的电流额定值。ADJ 管脚的阻抗输入较高 (200K)，容易受到其他来源的泄漏电流所影响。任何从这个管脚载下的电流，都会减低输出电流。为了避免出现任何电磁耦合情况，管脚的周遭设有保护线轨。

数量	零件参考	价值	描述	来源
1	R1	0.33Ω	电阻器, 1%, 0805	不同来源
1	C1,C2	150μF/20V	D 类 SMD 钽电容器	Kemet
1	C3	0.1μF/25V	SMD 0805 X7R	NIC 元件
1	C4	1μF/25V	SMD 1210 X7R	NIC 元件
1	L1	100μH	MSS6132-104	Coilcraft
1	U1	ZXLD1350	LED 驱动器 IC	ZETEX
1	U2	ZXSBMR16PT8	肖特基桥式整流器及续流二极管	ZETEX

表1 – 物料清单

从图 2 中的电路原理图可见，只需要使用 0Ω 电阻器，便可运用跳线连接，实现纯 DC 操作。
由于系统并没有反极性保护，所以用户要特别小心。

图 3 为电路设计，说明了节省空间和紧凑设计的优点。底层及顶层皆清楚显示，高效器件布置清晰可见。

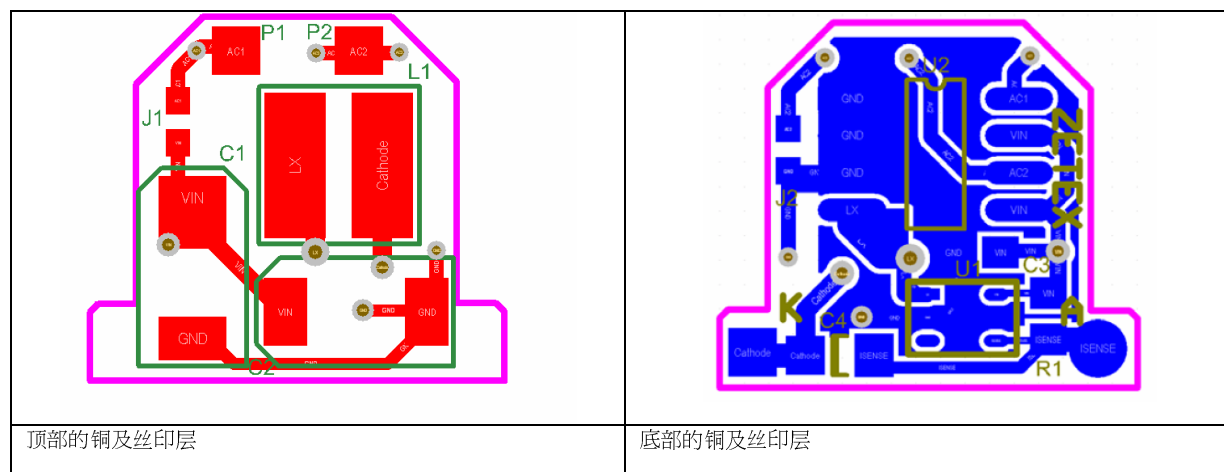


图 3：电路设计

主层设计建议如下：

- 所有薄器件设于同一边
- 以星形联结作为接地线轨
- 以接地环保护 ADJ 管脚
- 请检查：
 - 把 R1 连接至 ZXLD1350 愈短愈好 (感应线轨)
 - 滤波电容器 C3 应连接至最接近 V_{in} 管脚的地方
 - 续流电流路径愈短愈好，以保障系统的精密度和效率

电路板一览

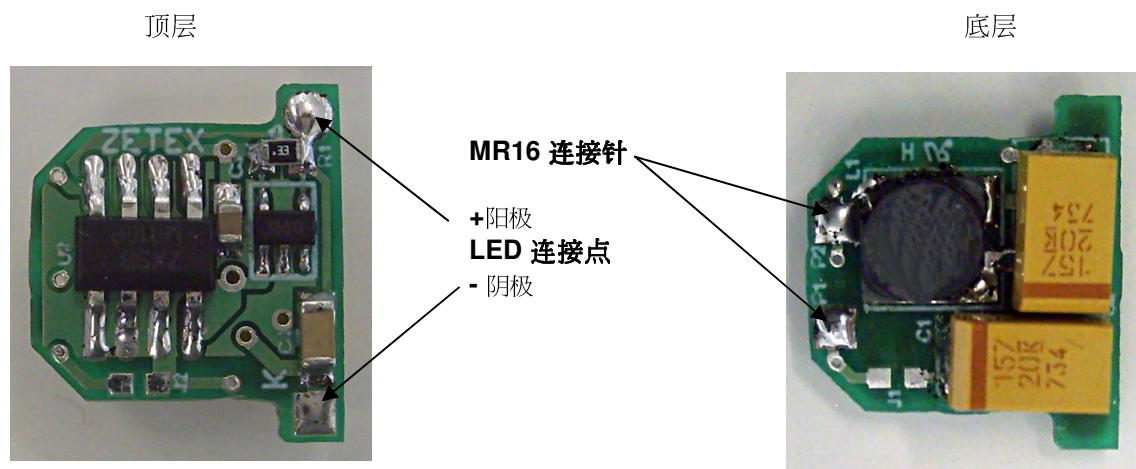


图 4：电路板一览

电感器的选择和开关电路佈线设计

电路中选用了 100 μH 的屏蔽式电感器，把标称频率设定于约 250kHz 的水平，同时把辐射电磁干扰减至最少。任何开关稳压器的设计，对减低辐射电磁干扰都相当重要。这款参考设计可以把关键的线轨长度减至最低，而关键性区域四周的接地面积则扩至最大。

电路的性能表现

电路的性能表现根据两项主要的参数进行评测，包括系统效率和电流精度。

参考电路的电流设定于 300mA 的标称值，但只须根据以下公式改变感应电阻器 R_{sense} ，电流便可调整至 350mA 或下的水平。

$$I_{\text{ref}} = 0.1 / R1 \quad [\text{A}]$$

当使用 $R1 = 0.33\Omega$ \rightarrow $I_{\text{ref}} = 300\text{mA}$

表 2 列出了 12V 至 15V DC 供应电压系统的相关资料，有关测试采用了肖特基二极管桥。最重要的参数包括系统效率及额定 LED 电流 (300mA) 和实际 LED 电流之间的误差。在 DC 环境下，频率介于 150kHz 和 300kHz 之间，视输入电压而定。不论输入电压多少，效率皆高于 87%，误差少于 2%。

输入电压 [V]	输入电流 [A]	输出电压 [V]	输出电流 [A]	效率	电流准确度
12.000	0.275	9.80	0.296	87.9%	1.3%
13.000	0.252	9.78	0.294	87.7%	2.0%
14.000	0.232	9.76	0.294	87.6%	2.0%
15.000	0.220	9.75	0.294	87.4%	2.0%

表 2 - DC 输入电压

表 3 列出了以一个采用 SMD 钽电容器及 AC 电磁变压器供电系统的相关资料。系统以节省空间为设计目标，同时避免使用体积更大、可靠性更低的电解电容器。对于体积、可靠性、成本及平均 LED 电流都有取舍，一般标定 12V AC 的变压器输出电压会变化 $\pm 10\%$ ，三个 LED 的压降约 10V，在图 8 可以看到，如电容值少于 200 μF ，AC 输入的波形扭歪了。当整流后电压没有被有效地平滑，谷低电压有可能低于 LED 电压，在这情况下，开关电路停止运作，LED 平均电流下降，最后 LED 输出流明也下降。

C1 [μF]	输入电压 [V]	输入电流 [A]	输出电压 [V]	输出电流 [A]	效率	电流准确度
100	12.70	0.303	9.28	0.225	54%	25%
150	12.60	0.394	9.50	0.271	52%	10%
200	12.53	0.432	9.55	0.293	52%	2%
300	12.50	0.386	9.70	0.295	60%	2%

表 3 - AC 输入电压

图 5 至图 8 显示由输入电容 $C_{in}=C_1+C_2+C_3$ 所影响的输入电压纹波及 LX 电压。输入电容愈大，输出电流愈准确，亦令平均输出流明愈高。当输入电容达 300 μF 时，整体表现，包括效率及电流准确度都最好。相反，当输入电容降低，输出电流准确度降低多达 25%，但效率总高于 50%。

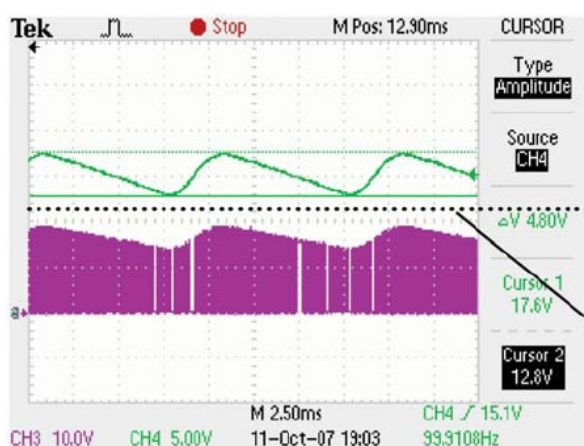


图 5 $C_{in}=300\mu\text{F}$



图 6 $C_{in}=200\mu\text{F}$

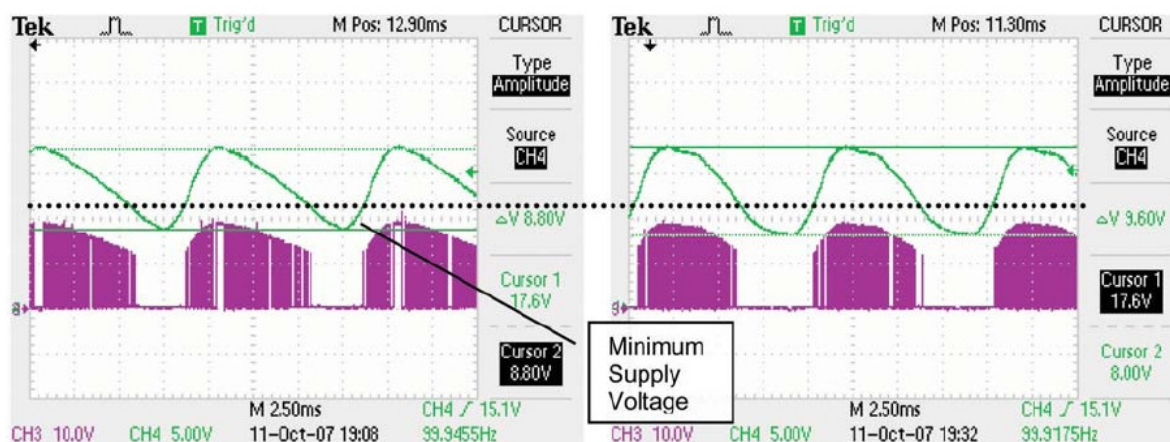
图 7 $C_{in}=150\mu F$ 图 8 $C_{in}=100\mu F$

图 5 至 8：输入纹波及 LX 电压 (Ch3 为 LX 管脚电压，Ch4 为输入电压)

有关 Gerber Plot 及进一步协助，可联络 Zetex 的本地销售代表。以下为各本地销售处的电邮地址。

europa.sales@zetex.com

usa.sales@zetex.com

asia.sales@zetex.com

结论

ZXLD1350 及 ZXSBMR16T8 配合其他被动元件，展现了一个细小、可靠、高效率及小元件数目的方案。这个超小设计可放进连接器的外壳，将这些对温度敏感的元素与发热的 LED 尽量分隔开。在最终的解决方案中，LED 电流及电容器的大小都要有所取舍，以达致最理想的效率、准确度、尺寸及元件数量。

这是一系列不同 MR16 解决方案和选项参考设计中的第一份设计手册。

Definitions**Product change**

Zetex Semiconductors reserves the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Zetex with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Zetex does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

Life support

Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written

approval of the Chief Executive Officer of Zetex Semiconductors plc. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

Terms and Conditions

All products are sold subjects to Zetex' terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Zetex sales office .

Quality of product

Zetex is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Zetex Semiconductors or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: www.zetex.com/salesnetwork

Zetex Semiconductors does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

Green compliance

Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

Product status key:

"Preview" Future device intended for production at some point. Samples may be available

"Active" Product status recommended for new designs

"Last time buy (LTB)" Device will be discontinued and last time buy period and delivery is in effect

"Not recommended for new designs" Device is still in production to support existing designs and production

"Obsolete" Production has been discontinued

Datasheet status key:

"Draft version" This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.

"Provisional version" This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance.

However, changes to the test conditions and specifications may occur, at any time and without notice.

"Issue" This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.

Europe	Americas	Asia Pacific	Corporate Headquarters
Zetex GmbH Streitfeldstraße 19 D-81673 München Germany	Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788 USA	Zetex (Asia Ltd) 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong	Zetex Semiconductors plc Zetex Technology Park, Chadderton Oldham, OL9 9LL United Kingdom
Telephone: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com	Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com	Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com	Telephone (44) 161 622 4444 Fax: (44) 161 622 4446 hq@zetex.com

These offices are supported by agents and distributors in major countries world-wide.

This publication is issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contact or be regarded as a representation relating to the products or services concerned. The company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.