

AN1149

Super Barrier Rectifiers (SBR[®]) improve Daytime Running Lamp (DRL) efficiency

Jason Huang, Diodes Automotive BU, Application Engineer
 Shane Timmons, Product Marketing Manager

Automotive lighting has been using LEDs for more than 10 years. Initially, one of the main driving forces behind adopting LEDs was the lumen per watt efficiency gains they offer over incandescent lamps. This meant that, to maximize the efficiency improvements, the focus was on lamps that are on most of the time. Other reasons include safety and, most recently, styling.

For example, the daytime running lamp or light (DRL) was introduced for the purposes of safety. These forward-facing lights remain illuminated, across all battery conditions, so that other road users can see the vehicle. The better efficiency of LEDs and their design flexibility allows automotive manufacturers to produce distinctively styled lighting - many cars are now instantly recognizable by their DRLs.

While LED technology offers vast improvements in performance, it is still important to consider an efficient power supply design. Buck-boost topology has been widely adopted for DRLs and Figure 1 shows a simplified circuit that typically employs a switching MOSFET (Q1) and, the focus for this document, a freewheeling or flywheel diode (D1) arrangement. Buck-boost topologies are normally implemented so that the correct drive of LEDs occurs across all input voltages – including cold cranking (9V or even down to 6V) and transients (>20V).

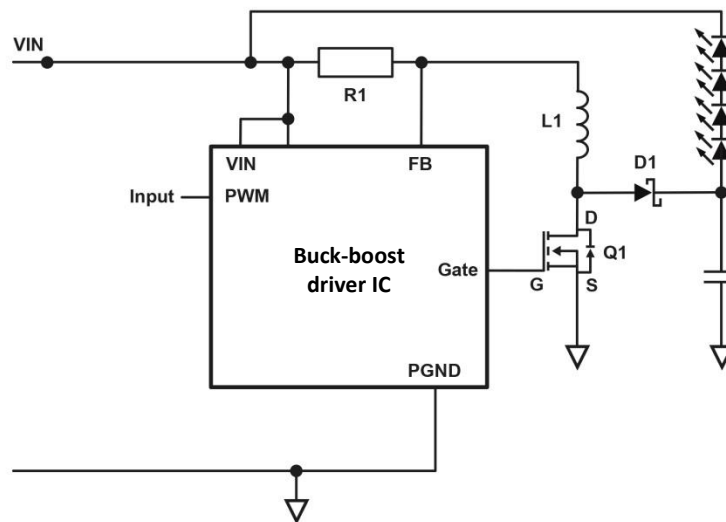


Figure 1. Simplified buck-boost DRL circuit

As this is a “boost” type of switching topology, the MOSFET and the freewheel diode peak currents will be much greater than the average LED current. This means careful choices must be made about the MOSFETs and freewheel diodes’ conduction and switching losses – especially at high temperatures.

This document demonstrates the performance improvements of using Super Barrier Rectifier (SBR[®]) technology in place of the typical Schottky diode technology in this automotive application.

SBR[®] is a Registered Trademark of Diodes Incorporated

SBR Introduction

Super Barrier Rectifier (SBR) is a proprietary and patented Diodes Incorporated technology that utilizes a Metal Oxide Semiconductor (MOS) manufacturing process to create a superior alternative to the Schottky diode. Internally, the device is effectively a MOSFET with its gate (G) and source (S) terminals internally connected together effectively becoming the diode anode terminal and the drain (D) becoming the cathode terminal, see Figure 2.

SBR devices are represented by the same electronic schematic symbol as the Schottky diode (Figure 3).

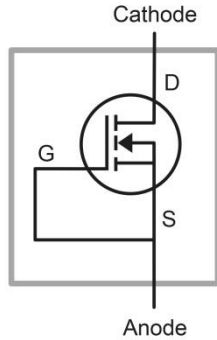


Figure 2. Simplistic representation of internal device and connections



Figure 3. SBR electronic schematic symbol

In every other way the device behaves as a diode and assures drop-in replacement compatibility. For example, a 10A, 100V Schottky can be replaced by the SBR equivalent device without concern for other components; however, immediate improvements in efficiency and reduced device case temperature can be realized.

Performance Evaluation

To demonstrate the performance improvements SBR brings over Schottky technology, we compare a leading competitor with the same rating, as shown in Table 1.

	Diodes Inc. SBR10M100P5Q	Competitor A 10A 100V rated
Device Technology	SBR	Schottky Diode
Typical Forward voltage $V_F(V)$ (I_F 1A @85°C)	0.50	0.50
Typical Forward voltage $V_F(V)$ (I_F 10A @85°C)	0.70	0.72
Typical leakage current $I_R(\mu A)$ @85°C	1.7	18
Typical leakage current $I_R(\mu A)$ @125°C	15	300
$E_{AS}(mJ)$	400	20
$I_{FSM}(A)$ (square,8.3ms/10ms)	220	200
Reverse Recovery Time t_{rr} (nS) ($I_F=3A$, $di/dt=50A/\mu s$, $V_R=50V@85^\circ C$)	28.3	33.2
Reverse Recovery Charge Q_{rr} (nC) ($I_F=3A$, $di/dt=50A/\mu s$, $V_R=50V@85^\circ C$)	9.4	14.1

Table 1. Forward and reverse characteristics of the devices

Using a buck-boost evaluation driver board (Figure 4), and running on a range of input voltages from 7V to 30V, each device is tested, at position D1, to drive a string of LEDs. Performance improvements are expected to be seen in the following areas:

1. Device case temperature
 - a. SBR technology remains cooler due to lower internal losses.
2. Power efficiency
 - a. Fast switching, low forward V_F , low reverse leakage current, low reverse recovery time and charge are all inherent with SBR technology and lead to improved efficiencies. These parameters remain more stable, compared with Schottky technology, at increased operational temperatures.

The efficiency of the driver board and case temperatures of each device were measured.

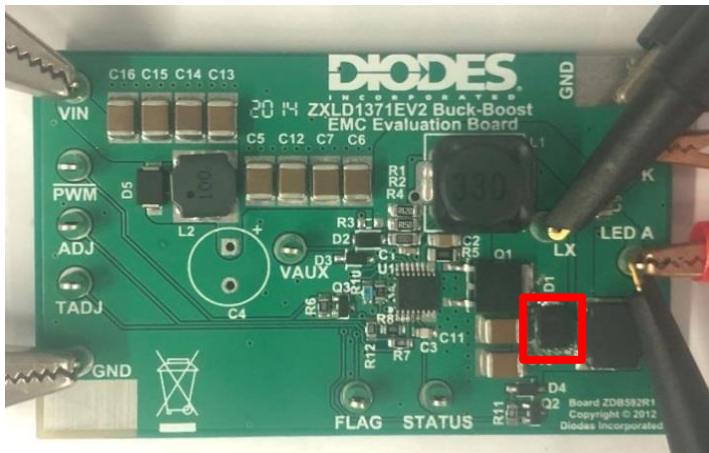


Figure 4. Each device tested in circuit at highlighted position D1

Ambient Temperature = 25°C

At 25°C both technologies provide high efficiency, with improvements of up to 3% for SBR reaching close to 92% overall, as shown in Figure 5.

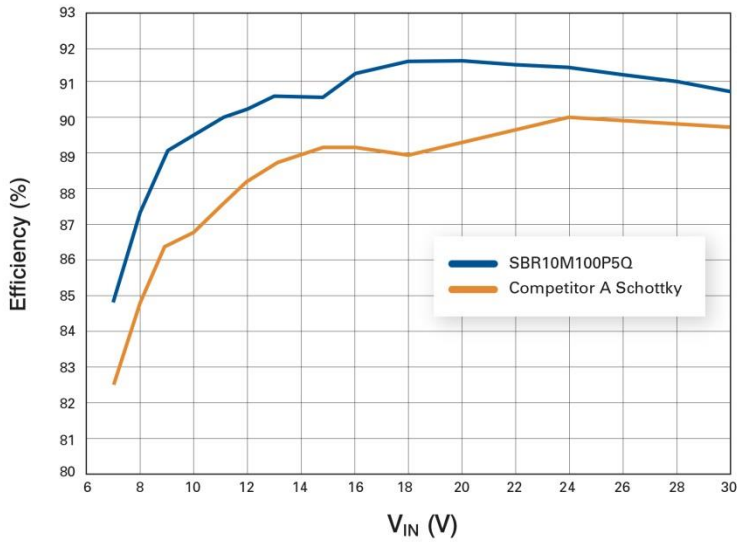


Figure 5. Buck-boost converter's efficiency with SBR vs. Schottky 25°C

Ambient Temperature = 85°C

At 85°C, however, significant efficiency drop-off of up to 6% can be seen with the Schottky device, as shown in Figure 6.

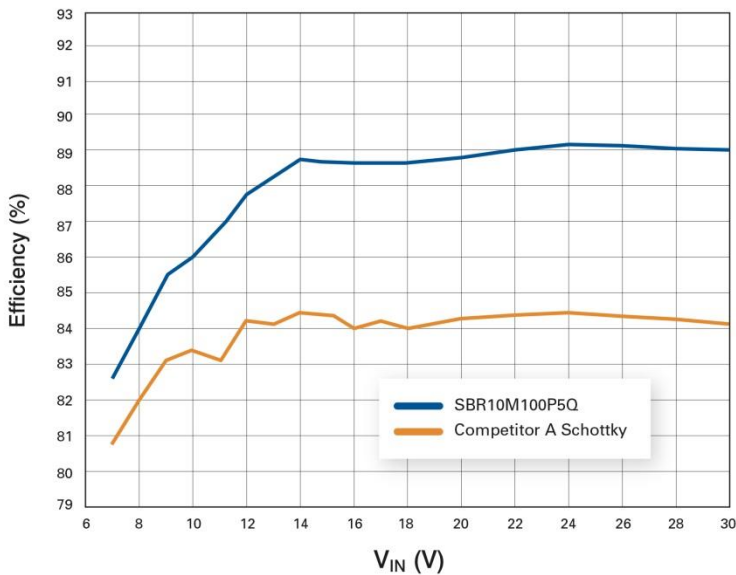


Figure 6. Buck-boost converter's efficiency with SBR vs. Schottky at 85°C

Device case temperatures

Despite the Schottky device having a large underside heatsink, the case temperature of the SBR consistently runs up to 5°C lower in temperature across a range of ambient temperatures, as can be seen in Figure 7.

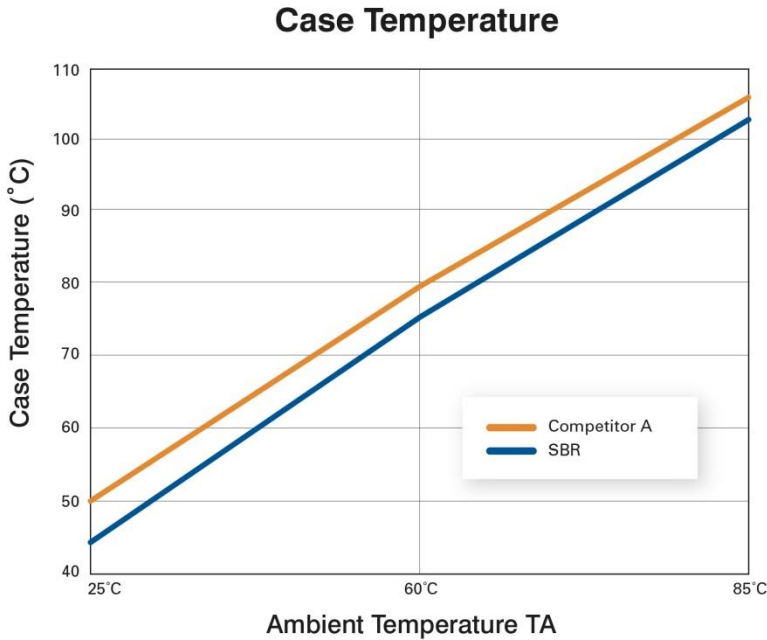


Figure 7. Case temperature vs. ambient temperature

Overall Efficiency

As the ambient temperature increases, the overall efficiency gap between the SBR and the Schottky device also increases, as can be seen in Figure 8. A combination of diode forward conduction losses, increased reverse leakage current and switching losses, in conjunction with the overall system losses, contribute to the differences seen as the ambient temperature rises.

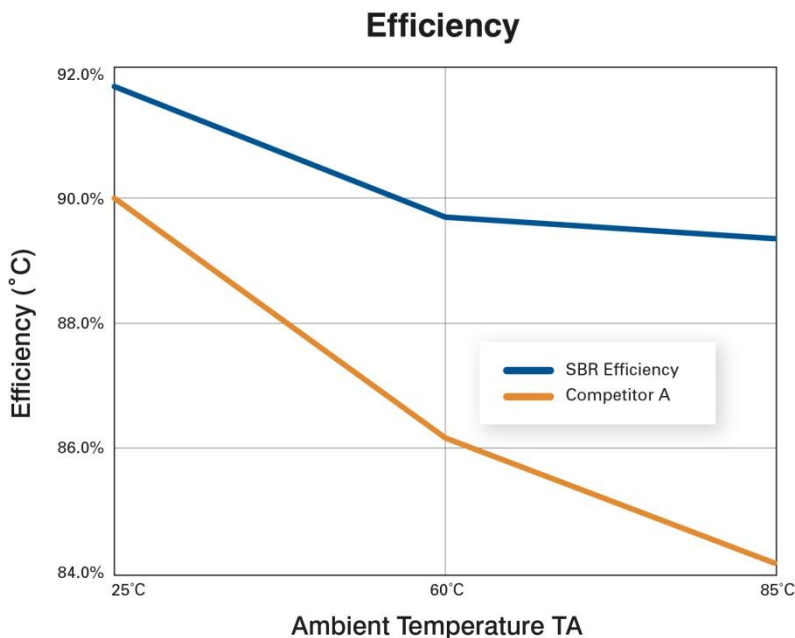


Figure 8. Efficiency vs. ambient temperature

Power saving

The overall result in improved efficiency is a saving in wasted power. Figure 9 shows that the improvement in efficiency returned a saving of up to 800mW.

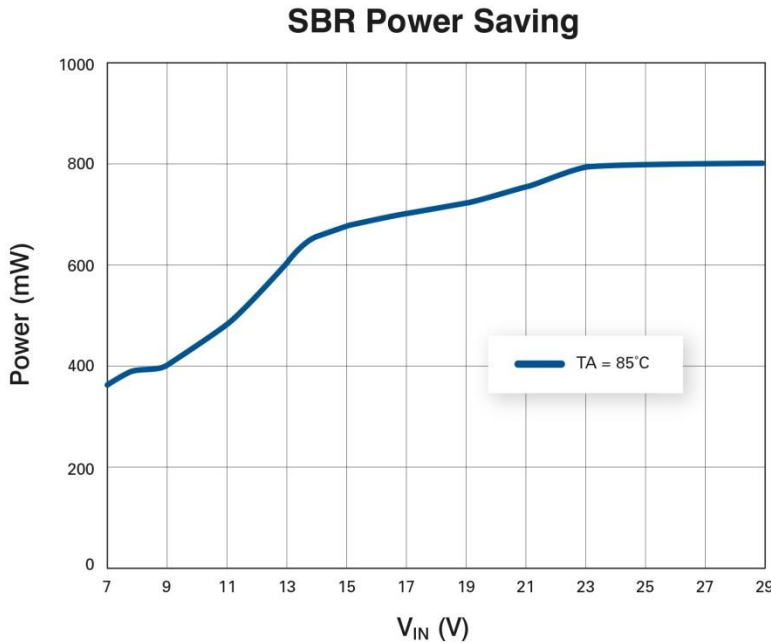


Figure 9. Power saving benefit of SBR vs. Schottky device at ambient temperature of 85°C

Conclusion

For some time Schottky technology has been selected for the freewheeling diode in typical buck-boost converters driving daytime running lamp LED lighting. The introduction of the SBR10M100P5Q, with its drop-in compatibility with Schottky diodes, means that circuit designers can now easily achieve lower losses due to faster switching times, lower forward voltage drop and lower reverse leakage current, leading to improvements in efficiency of up to 5%.

The lower operating temperatures, of up to 5°C, together with increased robustness for hotter ambient temperatures, give automotive customers extra confidence for long-term reliability and stability over Schottky diode technology. The reduced burden on thermal management systems also means further savings can be realized.

IMPORTANT NOTICE

DIODES INCORPORATED MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARDS TO THIS DOCUMENT, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION).

Diodes Incorporated and its subsidiaries reserve the right to make modifications, enhancements, improvements, corrections or other changes without further notice to this document and any product described herein. Diodes Incorporated does not assume any liability arising out of the application or use of this document or any product described herein; neither does Diodes Incorporated convey any license under its patent or trademark rights, nor the rights of others. Any Customer or user of this document or products described herein in such applications shall assume all risks of such use and will agree to hold Diodes Incorporated and all the companies whose products are represented on Diodes Incorporated website, harmless against all damages.

Diodes Incorporated does not warrant or accept any liability whatsoever in respect of any products purchased through unauthorized sales channel.

Should Customers purchase or use Diodes Incorporated products for any unintended or unauthorized application, Customers shall indemnify and hold Diodes Incorporated and its representatives harmless against all claims, damages, expenses, and attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized application.

Products described herein may be covered by one or more United States, international or foreign patents pending. Product names and markings noted herein may also be covered by one or more United States, international or foreign trademarks.

This document is written in English but may be translated into multiple languages for reference. Only the English version of this document is the final and determinative format released by Diodes Incorporated.

LIFE SUPPORT

Diodes Incorporated products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Diodes Incorporated. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body, or
2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Customers represent that they have all necessary expertise in the safety and regulatory ramifications of their life support devices or systems, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of Diodes Incorporated products in such safety-critical, life support devices or systems, notwithstanding any devices- or systems-related information or support that may be provided by Diodes Incorporated. Further, Customers must fully indemnify Diodes Incorporated and its representatives against any damages arising out of the use of Diodes Incorporated products in such safety-critical, life support devices or systems.

Copyright © 2019, Diodes Incorporated

www.diodes.com