

AN1196

Setting up Simplis Model to Change AL8890Q from Low- to High-Side Current Sensing

XueZheng Ding, Application Systems Manager, Diodes Incorporated

Introduction

The [AL8890](#) is a synchronous buck converter with internal compensation and switching frequency adjustable up to 2.5MHz. The device integrates a 120mΩ high-side power MOSFET and a 55mΩ low-side power MOSFET to provide high-efficiency DC-DC conversion. The AL8890 enables a continuous load current of up to 3.5A. The device features current-mode control operation, which enables easy loop stabilization to support a wide range of output loading.

The [ZXCT1009](#) is a high-side current sense monitor. Using this device eliminates the need to disrupt the ground plane when sensing a load current. It takes a high-side voltage developed across a current shunt resistor and translates it into a proportional output current. A user-defined output resistor scales the output current into a ground-referenced voltage.

The AL8890 is suitable for direct low-side current-sensing LED drivers requiring constant current output. To change to high-side current sensing, the AL8890 can add a high-side current-sense circuit (ZXCT1009) to change the topology from low-side to high-side; see Figure 1.

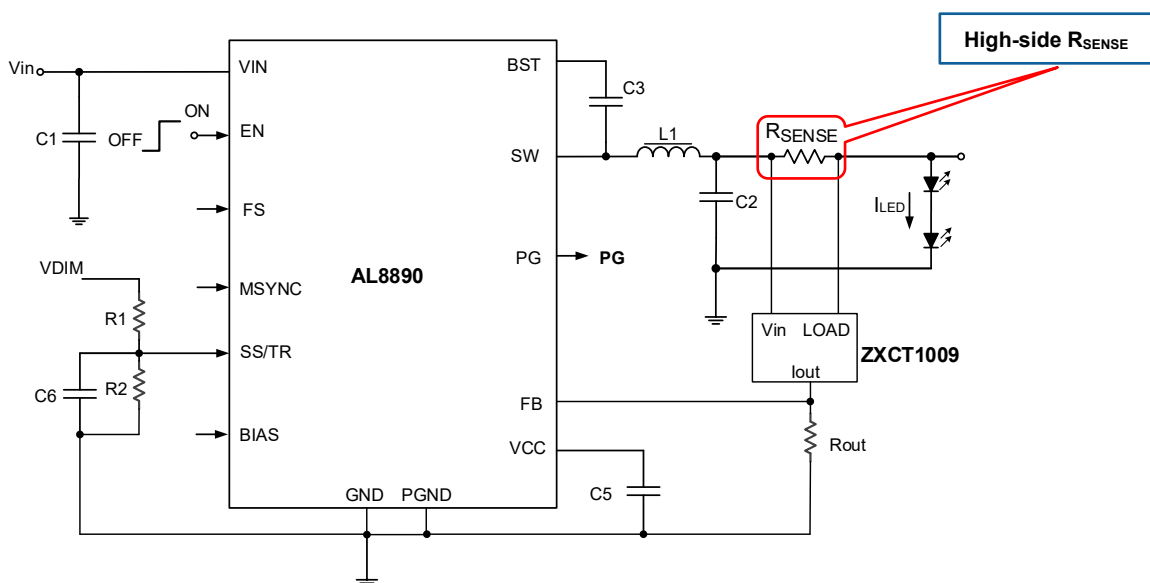


Figure 1. AL8890Q application circuit with ZXCT1009

Current-Sense Resistor

The current-sense resistor can be calculated as below:

$$R_{SENSE} = \frac{100 \times \frac{V_{FB}}{R_{OUT}}}{I_{LED}}$$

Where,

R_{SENSE} is the high-side current-sense resistor.

R_{OUT} is the resistor connect to the I_{OUT} pin of the ZXCT1009.

V_{FB} is the FB reference of the AL8890Q.

I_{LED} is the constant output current needed by the LED.

Input Capacitor

The input capacitor reduces the surge current drawn from the input supply and the switching noise from the device. The input capacitor must sustain the ripple current produced during the on-time on the upper MOSFET. Hence, it must have a low ESR to minimize the losses.

The RMS current rating of the input capacitor is a critical parameter that must be higher than the RMS input current. As a rule of thumb, select an input capacitor which has an RMS rating greater than half of the maximum load current.

Due to large di/dt through the input capacitors, electrolytic or ceramics should be used. If a tantalum must be used, it must be surge protected. Otherwise, capacitor failure may occur. For most applications, a 10 μ F ceramic capacitor is sufficient and a 0.1 μ F parallel capacitor is also recommended for improving stability.

Inductor

Calculating the inductor value is a critical factor in designing a buck converter. For most designs, the following equation can be used to calculate the inductor value:

$$L = \frac{V_{IN(TYP)}}{4 \times \Delta I_L \times f_{SW}}$$

Where ΔI_L is the inductor ripple current and f_{SW} is the buck converter switching frequency.

Choose the inductor ripple current to be 30% to 40% of the maximum load current. The maximum inductor peak current is calculated from:

$$I_{L(MAX)} = I_{LED} + \frac{\Delta I_L}{2}$$

Peak current determines the required saturation current rating, which influences the size of the inductor. Saturating the inductor decreases the converter efficiency while increasing the temperatures of the inductor and the internal MOSFETs. Hence, choosing an inductor with the appropriate saturation current rating is important.

To achieve the highest efficiency, the inductor's DC resistance should be as low as possible. Use a larger inductance for improved efficiency under light-load conditions.

Output Capacitor

The output capacitor value depends on the total series resistance of the LED string, r_D , and the switching frequency, f_{sw} . The capacitance required for the target LED ripple current is calculated using the equation below:

$$C_o = \frac{\Delta I_L}{8 \times f_{SW} \times r_D \times \Delta I_{LED}}$$

Where ΔI_{LED} is the maximum ripple current of I_{LED} .

SIMPLIS Simulation Set Up

Key parameters:

- $V_{IN}=24V$, $I_o=3.5A$ with 1-5 LEDs
- $F_{SW}=500kHz$
- $L=10\mu H$, $C_{OUT}=30\mu F$, $R_{SENSE}=22.8m\Omega$

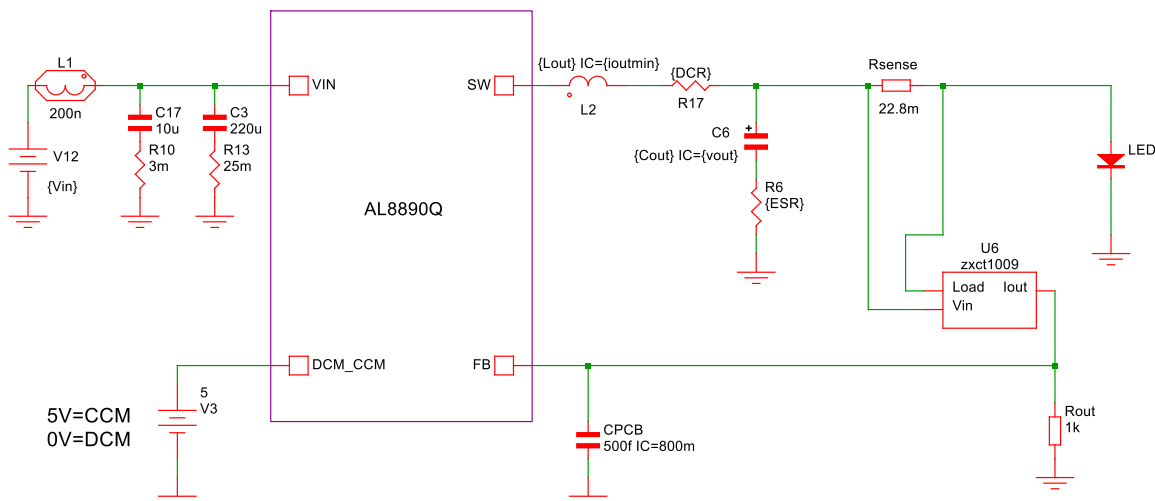


Figure 2. SIMPLIS schematic set up $I_o=3.5A$, AL8890Q with ZXCT1009

Simulation Results

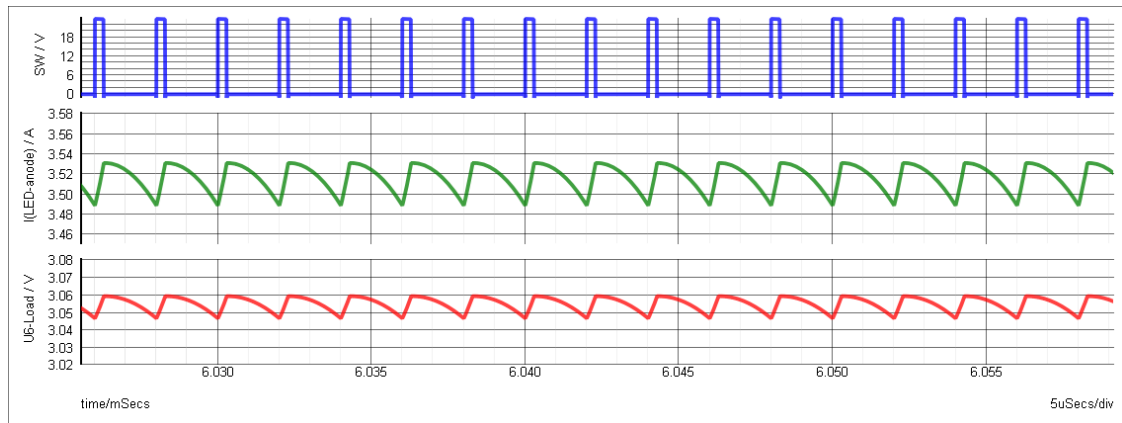


Figure 3. One LED load

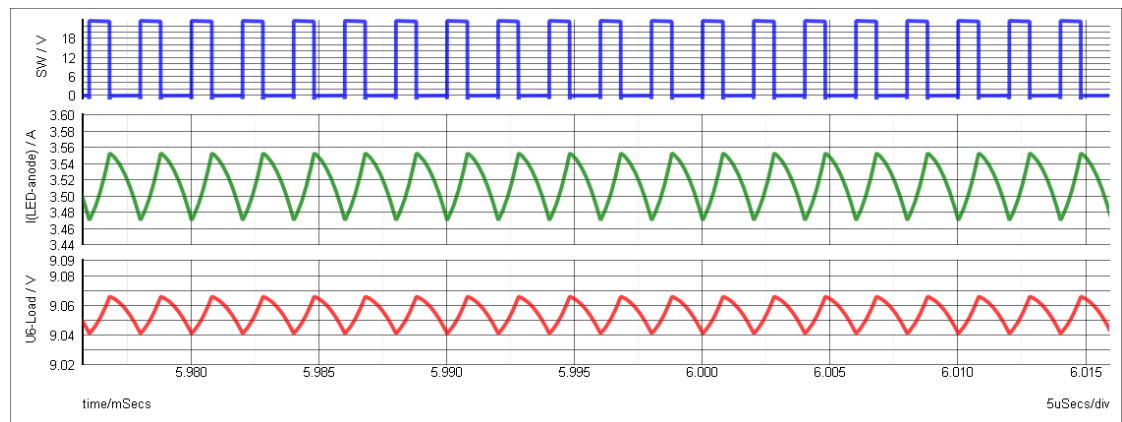


Figure 4. Three LED loads

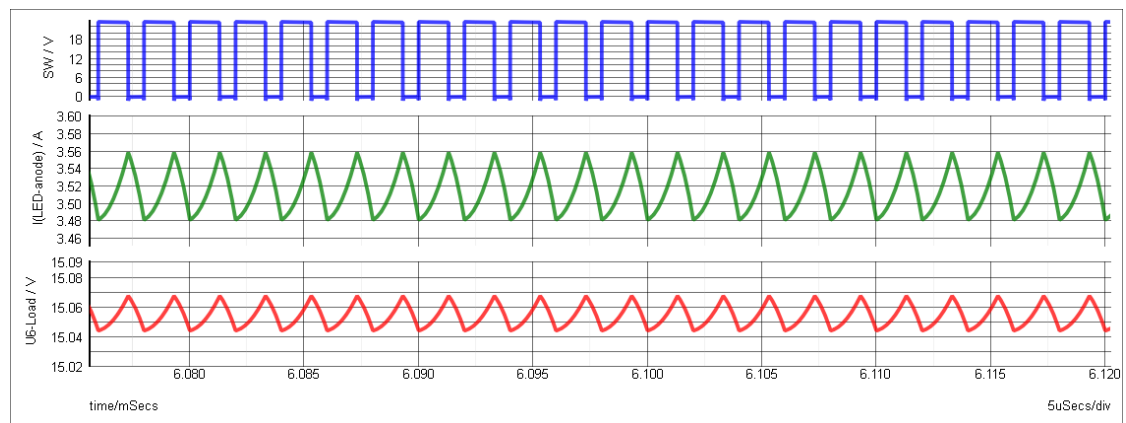


Figure 5. Five LED loads

IMPORTANT NOTICE

1. DIODES INCORPORATED (Diodes) AND ITS SUBSIDIARIES MAKE NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARDS TO ANY INFORMATION CONTAINED IN THIS DOCUMENT, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION).
2. The Information contained herein is for informational purpose only and is provided only to illustrate the operation of Diodes' products described herein and application examples. Diodes does not assume any liability arising out of the application or use of this document or any product described herein. This document is intended for skilled and technically trained engineering customers and users who design with Diodes' products. Diodes' products may be used to facilitate safety-related applications; however, in all instances customers and users are responsible for (a) selecting the appropriate Diodes products for their applications, (b) evaluating the suitability of Diodes' products for their intended applications, (c) ensuring their applications, which incorporate Diodes' products, comply the applicable legal and regulatory requirements as well as safety and functional-safety related standards, and (d) ensuring they design with appropriate safeguards (including testing, validation, quality control techniques, redundancy, malfunction prevention, and appropriate treatment for aging degradation) to minimize the risks associated with their applications.
3. Diodes assumes no liability for any application-related information, support, assistance or feedback that may be provided by Diodes from time to time. Any customer or user of this document or products described herein will assume all risks and liabilities associated with such use, and will hold Diodes and all companies whose products are represented herein or on Diodes' websites, harmless against all damages and liabilities.
4. Products described herein may be covered by one or more United States, international or foreign patents and pending patent applications. Product names and markings noted herein may also be covered by one or more United States, international or foreign trademarks and trademark applications. Diodes does not convey any license under any of its intellectual property rights or the rights of any third parties (including third parties whose products and services may be described in this document or on Diodes' website) under this document.
5. Diodes' products are provided subject to Diodes' Standard Terms and Conditions of Sale (<https://www.diodes.com/about/company/terms-and-conditions/terms-and-conditions-of-sales/>) or other applicable terms. This document does not alter or expand the applicable warranties provided by Diodes. Diodes does not warrant or accept any liability whatsoever in respect of any products purchased through unauthorized sales channel.
6. Diodes' products and technology may not be used for or incorporated into any products or systems whose manufacture, use or sale is prohibited under any applicable laws and regulations. Should customers or users use Diodes' products in contravention of any applicable laws or regulations, or for any unintended or unauthorized application, customers and users will (a) be solely responsible for any damages, losses or penalties arising in connection therewith or as a result thereof, and (b) indemnify and hold Diodes and its representatives and agents harmless against any and all claims, damages, expenses, and attorney fees arising out of, directly or indirectly, any claim relating to any noncompliance with the applicable laws and regulations, as well as any unintended or unauthorized application.
7. While efforts have been made to ensure the information contained in this document is accurate, complete and current, it may contain technical inaccuracies, omissions and typographical errors. Diodes does not warrant that information contained in this document is error-free and Diodes is under no obligation to update or otherwise correct this information. Notwithstanding the foregoing, Diodes reserves the right to make modifications, enhancements, improvements, corrections or other changes without further notice to this document and any product described herein. This document is written in English but may be translated into multiple languages for reference. Only the English version of this document is the final and determinative format released by Diodes.
8. Any unauthorized copying, modification, distribution, transmission, display or other use of this document (or any portion hereof) is prohibited. Diodes assumes no responsibility for any losses incurred by the customers or users or any third parties arising from any such unauthorized use.
9. This Notice may be periodically updated with the most recent version available at <https://www.diodes.com/about/company/terms-and-conditions/important-notice>

The Diodes logo is a registered trademark of Diodes Incorporated in the United States and other countries.
All other trademarks are the property of their respective owners.
© 2025 Diodes Incorporated. All Rights Reserved.

www.diodes.com