

AN59

Designing with Shunt Regulators - Series regulation

Peter Abiodun A. Bode, Snr. Applications Engineer, Diodes Incorporated


Introduction

Series regulators are versatile means of supplying power to many types of electronic circuits. Although both fixed and adjustable regulators are readily available off the shelf at competitive prices, there are instances when it may be desirable or necessary to design a discrete solution.

Such reasons might be due to requirement for a more accurate source than is commercially available - i.e. a precision regulator. These might be for instrumentation, calibration or environmental reasons. Low noise or level of required power might be other possible reasons for seeking a discrete solution.

The Zetex precision references can make implementation of these discrete solutions relatively simple. This document details the design considerations of the series regulator.

Basic Series Regulator

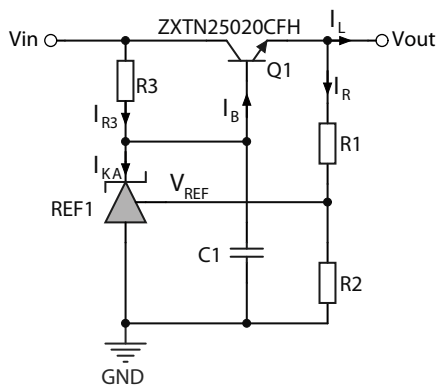

$$V_{OUT} = V_{REF} \left(1 + \frac{R1}{R2} \right)$$

$$R3 = \frac{V_{IN(min)} - (V_{OUT} + V_{BE(max)})}{I_{R3}}$$

$$(I_{B(max)} + I_{KA(min)}) \leq I_{R3} \leq I_{KA(max)}$$

Figure 1 Basic series regulator using a reference

A series regulator has the advantage that the series element (Q1) has a different voltage across it from that across the load. This voltage can be arranged to be very low in comparison leading to a much lower power dissipation in the series element, Q1, than is being delivered to the load. In addition, There is little or no power dissipation in Q1 if there is no load (i.e. when $I_L = 0$) other than the very small current due to I_R . These are the reasons why it is a better method for medium/high power applications than the shunt regulator alone.

It is an irony and a practical benefit that the most important basic building block of a series regulator is a shunt regulator which can be readily identified in Figure 1. The series regulator is, at most, only as good as the quality of this shunt regulator which, in its crudest form, could be a zener diode. The function of the shunt regulator is not to power the load but to drive the transistor which powers the load. As long as Q1 is suitably sized, this simple circuit can be configured to supply very high power and current running into several 10's of amperes and hundreds of Watts.

Q1 could be a single device as shown or it could be a Darlington pair or even several transistors in parallel as the need may be.

Accuracy

The accuracy of the circuit is affected only by three components: the tolerance of the reference and that of resistors R1 and R2. See Appendix in AN57 for further information on this.

Calculated Example 1

Requirement

Supply Voltage: 12V to 15V

Output voltage: 10V \pm 1%

Load current: 100mA

Assume the use of TLV431.

Discussion

The ZXTN25020CFH transistor is used in this example because it offers a high forward gain (180 - 500) and a fairly high power handling capability (1.25W) for a device in a SOT23 package.

The equations for determining R1, R2 and accuracy are the same as in all reference applications. The objective here is to determine R1, R2 and R3 and check that the transistor Q1 can handle any resultant power dissipation.

Solution

R1 and R2 are chosen to be high enough in value that significant power is not wasted. On the other hand they need to be low enough that regulation accuracy and stability are achieved. Either R1 or R2 can be arbitrarily fixed and the other calculated from

$$V_{OUT} = V_{REF} \left(1 + \frac{R1}{R2} \right) \quad \text{Equation 1}$$

AN57 showed the benefit of choosing a value of R1 in the region of 100kohm. Assume R1 is 100k and rearrange Equation 1 to obtain

$$R2 = \frac{R1}{\left(\frac{V_{OUT}}{V_{REF}} - 1 \right)}$$

$$R2 = \frac{100k}{\left(\frac{10}{1.24} - 1 \right)}$$

$$= 14.15k$$

Or

$$R2 = 14.2k$$

to the nearest E192 value
and within 0.35%.

Determine maximum required base current, $I_{B(max)}$

$$I_{B(max)} = \frac{I_{OUT(max)}}{h_{FE(min)} + 1}$$

$$= \frac{100mA}{181}$$

Hence,

$$I_{B(max)} = 552.5\mu A$$

This is the maximum base current required by the transistor. R3 needs to be able to supply this plus, at least, the minimum cathode current for the TLV431 which is 100 μ A.

Therefore,

$$I_{R3(\min)} = 652.5\mu A$$

$$R3 = \frac{V_{IN(\min)} - (V_{OUT} + V_{BE(\max)})}{I_{R3(\min)}}$$

$$R3 = \frac{12 - (10 + 0.9)}{652.5\mu A}$$

$$= 1.68 \text{ k}\Omega$$

Or

$$1.6 \text{ k}\Omega$$

to the nearest lower E24 value.

Off-load and at maximum input, all of I_{R3} will flow into the TLV431 and it is necessary to check that this current will not be excessive.

Hence,

$$I_{R3(\max)} = \frac{V_{IN(\max)} - (V_{OUT} + V_{BE(\min)})}{R3}$$

$$\frac{15 - 10.6}{1600}$$

$$= 2.75\text{mA}$$

less than 15mA as required.

The last thing to check is that the transistor is suitably power-rated for this application.

Hence,

$$P_{Q1(\max)} = (V_{IN(\max)} - V_{OUT}) \cdot \left(\frac{h_{FE(\max)}}{h_{FE(\max)} + 1} \right) I_{OUT}$$

$$= (15 - 10) \cdot 0.998 \cdot 0.1$$

$$= 0.5\text{W}$$

This is comfortably within the capability of the ZXTN25020CFH when suitably mounted.

Accuracy

It is necessary to determine the required component tolerances for meeting the specified accuracy. Since the design calls for an accuracy of $\pm 1\%$, it follows that the TLV431 used must be the 0.5% tolerance part. The resistors' tolerance can then be calculated as follows (see AN57 Shunt Regulators for more information):

First determine α_{RD}

$$\alpha_{RD} = \left(\frac{R1}{R1 + R2} \right) (\alpha_{R1} - \alpha_{R2})$$

This is the error caused by using preferred resistors as opposed to calculated values.

$$\alpha_{RD} = \left(\frac{100k}{100k + 14.15k} \right) (0 - 0.35)$$

$$\alpha_{RD} = -0.31\%$$

R1, R2 tolerance,

$$\alpha_R = \pm \left[\left(\frac{\alpha_{VOUT} - (\alpha_{TLV431} + \alpha_{RD})}{2} \right) \left(\frac{R1 + R2}{R1} \right) \right]$$

$$\alpha_R = \pm \left[\left(\frac{1 - (0.5 - 0.31)}{2} \right) \left(\frac{114.2}{100} \right) \right]$$

$$\alpha_R = \pm 0.463\%$$

Summary

Using a TLV431B, R1 = 100k, R2 = 14.2k (both 0.463% or better) and R3 = 1.6k will satisfy the requirement.

Series Regulator with Current Limit

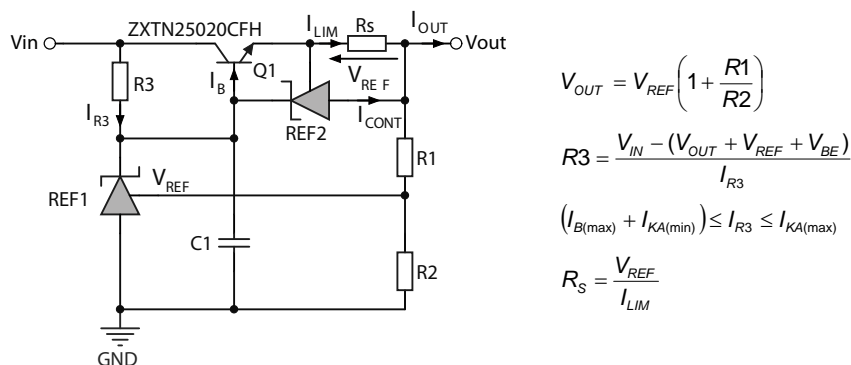


Figure 2 Series regulator with current limit

The circuit in Figure 1 has no current limit. If a short circuit were to be applied to the output, the resultant current, I_{SC} , that would flow can potentially be

$$I_{SC} = (h_{FE(max)} + 1) \left(\frac{V_{IN(max)} - V_{BE}}{R3} \right) = (501) \left(\frac{15 - 0.9}{1600} \right)$$

$$I_{SC} = 4.4A$$

The ZXTN25020CFH, with its IC(cont) rating of 4.5A could handle this current. A much more serious issue is that all of the supply voltage now appears across Q1 at the same time. At 15V this amounts to a power dissipation of 66W. According to the Pulse Power Dissipation chart in the ZXTN25020CFH datasheet, the transistor will fail in less than 0.3ms if subjected to this level of power.

Figure 2 adds current limit to the series regulator in Figure 1 using a second reference (REF2), also a TLV431. For currents below the limit, the circuit works normally supplying the required load current at the design voltage. However, should attempts be made to exceed the design current set by REF2, the device begins to shunt current away from the base of Q1. This begins to reduce the output voltage and thus ensuring that the output current is clamped at the design value. Subject only to Q1's ability to withstand the resulting power dissipation, the circuit can withstand either a brief or indefinite short circuit.

Calculated Example 2

Requirement

Add a 105mA $\pm 5\%$ current limit to Calculated Example 1 (Figure 1 Basic series regulator).

Solution

$$R_S = \frac{V_{REF}}{I_{LIM}}$$

$$= \frac{1.24}{0.105}$$

$$= 11.81$$

or

$$R_S = 11.8 \Omega$$

To nearest E48 value.

Using a 1% device (TLV431A), an R_S value of 11.8Ω 1% makes the worst case cumulative error 2%, within $\pm 5\%$ as required.

Determination of actual short circuit current

When the current limit circuit is operative, the output current consists of two components as shown below. I_{LIM} remains constant, I_{CONT} varies continuously with the level of overload until reaching a maximum at full short circuit i.e. when $V_{OUT} = 0$.

$$\begin{aligned} \text{Hence} \quad I_{OUT(max)} &= I_{LIM} + I_{CONT} \\ &= I_{LIM} + \left(\frac{V_{IN(max)} - (V_{REF} + V_{BE})}{R3} - \frac{I_{LIM}}{h_{FE} + 1} \right) \\ &= I_{LIM} \left(\frac{h_{FE}}{h_{FE} + 1} \right) + \frac{V_{IN(max)} - (V_{REF} + V_{BE})}{R3} \\ &\approx I_{LIM} + \frac{V_{IN(max)} - (V_{REF} + V_{BE})}{R3} \quad \text{since } h_{FE} \gg 1 \end{aligned}$$

$$\begin{aligned} \text{Therefore,} \quad I_{OUT(max)} &= \frac{1.24}{11.8} + \frac{15 - (1.24 + 0.6)}{1600} \\ I_{OUT(max)} &= 113.3\text{mA} \end{aligned}$$

This represents the maximum short circuit current, it is not the current seen by transistor Q1 which is given by

$$\begin{aligned} I_C &= I_{LIM} \left(\frac{h_{FE}}{1 + h_{FE}} \right) \\ &\approx I_{LIM} \quad \text{if } h_{FE} \gg 1 \\ \text{Therefore} \quad I_C &= 105\text{mA} \end{aligned}$$

This means that a direct short circuit would not immediately result in a failure. It is still however necessary to estimate how long the circuit could withstand such an overload condition for as follows.

Overload duration

With a short circuit, the current will be limited to a maximum of 107mA (105 +2%). Worst case voltage across Q1 will be 13.76V (i.e. 15V - 1.24V). Therefore, Q1's dissipation will be 1.47W. Referring to the Pulse Power Dissipation chart in the ZXTN25020CFH datasheet, it can be seen that Q1 will withstand this condition for between 10s and 100s. This is if there is a direct short circuit of the output voltage. If there is only a partial overload, the situation will be far less severe.

There are a number of steps that can be taken if an indefinite short circuit handling capability is required. The simplest action would be to use a slightly bigger transistor for Q1. For example, the ZXTN2005G is a transistor in a SOT223 package and will dissipate up to 3W continuously when suitably mounted.

Another method that could be used is to apply a re-entrant or "fold-back" current limiting rather than the simple current limiting above. This is a method which adjusts the over-load current limit according to the value of the output voltage such that, by the time the output voltage drops to zero - i.e. a short circuit, the current limit has dropped to a very small value, typically 5% or less of the full load current. This is a more complex solution and is outside the scope of this document.

Conclusion

Precision series regulators can be implemented using references. These allow the user to have more control of both the qualitative (e.g. accuracy) and quantitative (e.g. output voltage, current limit or power delivery) to suit the application.

Recommended further reading

AN58 - Designing with Shunt Regulators - *Shunt Regulation*

AN60 - Designing with Shunt Regulators - *Fixed Regulators and Opto-Isolation*

AN61 - Designing with Shunt Regulators - *Extending the operating voltage range*

AN62 - Designing with Shunt Regulators - *Other Applications*

AN63 - Designing with Shunt Regulators - *ZXRE060 Low Voltage Regulator*

Intentionally left blank

Definitions

Product change

Diodes Incorporated reserves the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Diodes Inc. with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Diodes Inc. does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

Life support

Diodes Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Diodes Incorporated. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

Terms and Conditions

All products are sold subjects to Diodes Inc. terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Diodes Zetex sales office.

Quality of product

Diodes Zetex Semiconductors Limited is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Diodes Inc. or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: www.zetex.com or www.diodes.com

Diodes Inc. does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

Green compliance

Diodes Inc. is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Diodes Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

Product status key:

"Preview"	Future device intended for production at some point. Samples may be available
"Active"	Product status recommended for new designs
"Last time buy (LTB)"	Device will be discontinued and last time buy period and delivery is in effect
"Not recommended for new designs"	Device is still in production to support existing designs and production
"Obsolete"	Production has been discontinued

Datasheet status key:

"Draft version"	This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.
"Provisional version"	This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice.
"Issue"	This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.

Diodes Zetex sales offices

Europe	Americas	Asia Pacific	Corporate Headquarters
Diodes Zetex GmbH Kustermann-park Balanstraße 59 D-81541 München Germany Telephone: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com	Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788 USA Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com	Diodes Zetex (Asia) Ltd 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com	Diodes Incorporated 15660 N Dallas Parkway Suite 850, Dallas TX75248, USA Telephone: (1) 972 385 2810 www.diodes.com

© 2008 Published by Diodes Incorporated