

AN66

Designing with shunt regulators – AC amplifier

Peter Abiodun A. Bode, Snr. Applications Engineer, Diodes Incorporated

Introduction

A three terminal shunt regulator can be used to make a simple and effective single-supply AC amplifier. The solution offers cost and space saving advantages. This application note presents the details.

The amplifier

The amplifier is shown in Figure 1. The DC gain is set by R1,R2. R3 sets up reference/load current which is its normal function. The input and output from the amplifier are necessarily AC coupled by C1 and C2 respectively.

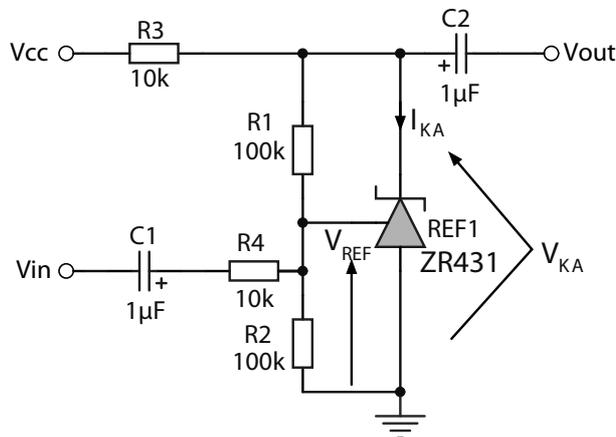


Figure 1 - Gain of 10 amplifier using a 3-terminal shunt regulator

The gain calculation uses the principle that the reference terminal voltage of the shunt regulator is fixed by the feedback network and also draws negligible current. Hence a change in V_{IN} produces equal current change in R4 and R1.

$$\Delta I_{IN} = \frac{\Delta V_{IN}}{R4} = - \frac{\Delta V_{OUT}}{R1}$$

Therefore the AC gain within the pass band, G_{AC} , is given by,

$$G_{AC} = \frac{\Delta V_{OUT}}{\Delta V_{IN}} = - \frac{R1}{R4}$$

Design procedure

1. Set up DC conditions

- a. Choose V_{CC} from $(2 \cdot V_{REF} + V_{KA(min)}) < V_{CC} \leq (V_{OUT(pk-pk)} + V_{KA(min)})$
- b. Choose R2. A value of the order of 100k and up is recommended.

AN66

c. Calculate R1 from

$$R1 = R2 \cdot \left(\frac{V_{CC} - V_{KA(\min)}}{2 \cdot V_{REF}} - 1 \right)$$

This ensures that V_{KA} is biased at half of V_{CC} .

d. Determine maximum load (minimum R_{LOAD}) on the output and calculate R3 from

$$R3 \leq \left(\frac{V_{CC} + V_{KA(\min)}}{2 \cdot V_{OUT(pk-pk)}} \cdot R_{LOAD(\min)} \right)$$

2. Set up AC conditions

a. Determine R4 from $R4 = \frac{R1}{G_{AC}}$ where G_{AC} is the required AC gain.

R4, R1 and R2 can be scaled up or down to obtain a desired impedance gain

b. Determine the 6dB (low corner frequency cut-off) point of the amplifier, f_{CL} , and calculate C1 from

$$C1 \geq \frac{1}{2 \cdot \pi \cdot f_{CL} \cdot R4}$$

c. Calculate C2 from

$$C2 \geq \frac{1}{2 \cdot \pi \cdot f_{CL} \cdot R_{LOAD(\min)}}$$

Note that $V_{KA(\min)}$ is usually not a quantified parameter for shunt regulators. However it is usually less than 1.5V for most devices.

Input impedance

If the design steps above have been followed, then the input impedance, Z_{IN} , is given by $Z_{IN} \approx R4$. The user therefore has full control of the input impedance.

Output impedance

The output impedance of the amplifier, Z_{OUT} , provided the design steps above have been followed, is the dynamic slope resistance of the reference used and given by $Z_{OUT} \approx R_Z$. R_Z for most references is typically a few hundred milliohms and therefore will not be a problem in most applications.

Bandwidth

The amplifier behave like an operational amplifier in that it has a constant Gain-Bandwidth Product (GBP). In a practical test carried out using the ZR431, a GBP of 1MHz was obtained. This will vary depending on which device is used.

Drive capability

The shunt regulator amplifier, by definition, is a Class A amplifier. This means that, even when it is not delivering power, it is consuming 50% of the total available power. It is therefore best suited for signal or low power applications such as driving earphones or headphones.

Nevertheless, the amplifier's peak-to-peak current drive capability is quantified by the $I_{KA(max)}$ rating of the shunt regulator. If the application demands it, this rating can be boosted by an external transistor as shown below. Refer to AN57 for details on current-boosting a shunt regulator.

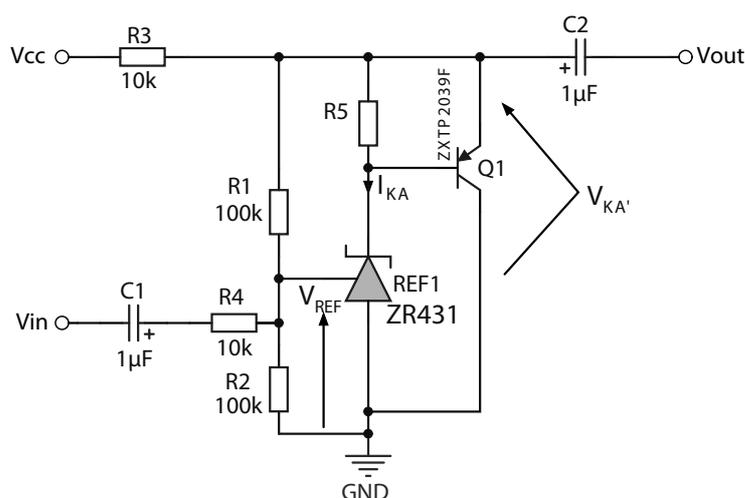


Figure 2 - Gain of 10 shunt regulator amplifier with current-boosted output

Stability

Some shunt regulators can become unstable when only lightly loaded. In this case it may be necessary to preload the output with a resistor in order to maintain this minimum load requirement. Doing this modifies $R_{LOAD(min)}$ and it is this modified $R_{LOAD(min)}$ that should be used in the procedure when calculating $R3$ and $C2$.

Simplified circuit

If the output voltage requirement is within V_{REF} and $V_{KA(min)}$ of the shunt regulator, i.e. $V_{OUT(pk-pk)} \leq (V_{REF} - V_{KA(min)})$, then the simplified circuit below may be used instead. This circuit gets rid

AN66

of R2 to give the amplifier a unity DC gain. The AC gain remains the same being determined by R1/R4.

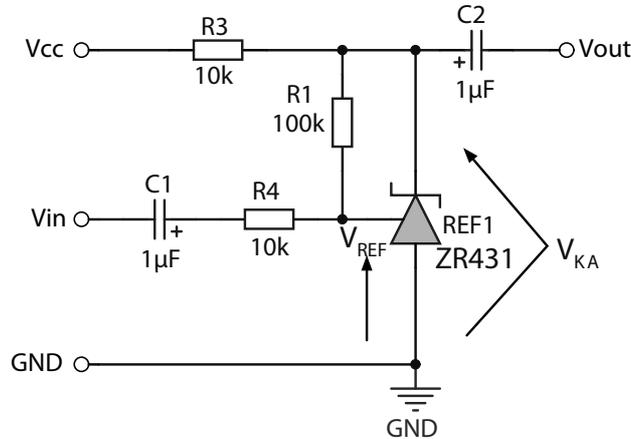


Figure 3 - Gain of 10 amplifier with unity DC gain

Bench Tests

The circuit in Figure 1 was built using the ZR431 shunt regulator. The following graphs show the obtained performance. In all cases, the top trace is the input and the bottom trace output.

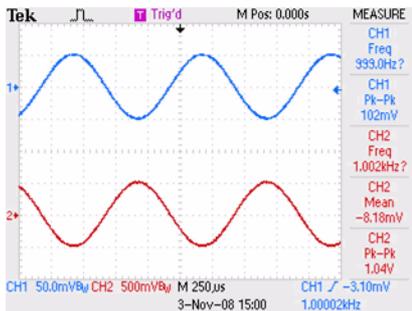


Figure 4 $G = 10$, $V_{IN} = 50\text{mV}$ 1kHz sine wave, load = 10k

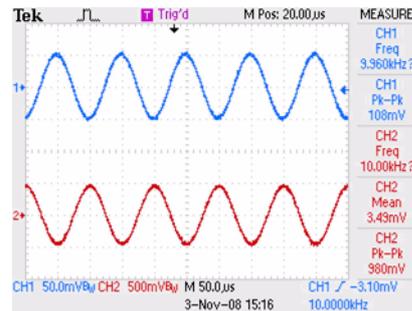


Figure 5 $G = 10$, $V_{IN} = 50\text{mV}$ 10kHz sine wave, load = 200R

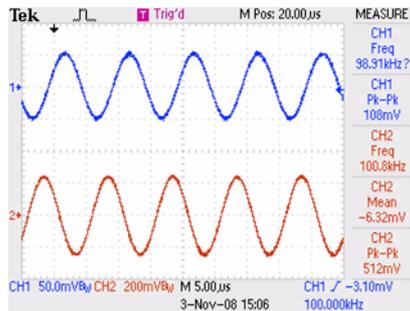


Figure 6 $G = 10$, $V_{IN} = 50\text{mV}$ 100kHz sine wave, load = 10k

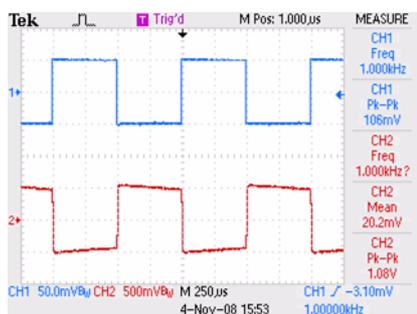


Figure 7 $G = 10$, $V_{IN} = 50mV$ 1kHz square wave,
load = 10k

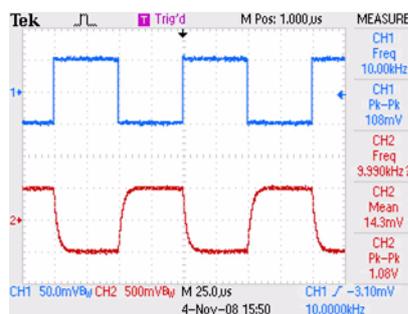


Figure 8 $G = 10$, $V_{IN} = 50mV$ 10kHz square wave,
load = 10k

The graph below shows test result for Figure 3.

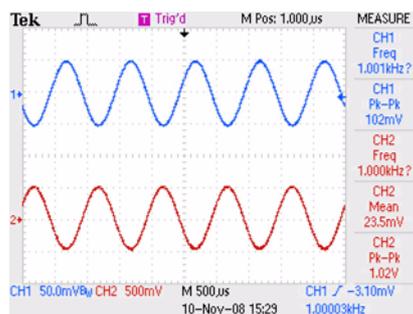


Figure 9 $G = 10$, $V_{IN} = 50mV$ 1kHz sine wave, load = 10k

Conclusion

This application note has shown that a shunt regulator can be used as an AC amplifier and that it offers practical benefits in terms of parts rationalisation, space and cost savings.

Recommended further reading

AN67 - Designing with Shunt Regulators – *mixing, adding or summing*

AN57 - Designing with Shunt Regulators – *Shunt Regulation*

AN58 - Designing with Shunt Regulators – *Series Regulation*

AN59 - Designing with Shunt Regulators – *Fixed Regulators and Opto-Isolation*

AN60 - Designing with Shunt Regulators – *Extending the operating voltage range*

AN61 - Designing with Shunt Regulators – *Other Applications*

AN62 - Designing with Shunt Regulators – *ZXRE060 Low Voltage Regulator*

AN66

Definitions

Product change

Diodes Incorporated the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Diodes Inc. with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Diodes Inc. does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

Life support

Diodes Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Diodes Incorporated. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

Terms and Conditions

All products are sold subjects to Diodes Inc. terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Diodes' sales office .

Quality of product

Diodes Zetex Semiconductors Limited is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Diodes Inc. or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: www.diodes.com

Diodes Zetex does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

Green compliance

Diodes Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Diodes Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

Product status key:

"Preview"	Future device intended for production at some point. Samples may be available
"Active"	Product status recommended for new designs
"Last time buy (LTB)"	Device will be discontinued and last time buy period and delivery is in effect
"Not recommended for new designs"	Device is still in production to support existing designs and production
"Obsolete"	Production has been discontinued

Datasheet status key:

"Draft version"	This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.
"Provisional version"	This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice.
"Issue"	This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.

Sales offices

The Americas	Europe	Taiwan	Shanghai	Shenzhen	Korea
3050 E. Hillcrest Drive Westlake Village, CA 91362-3154 Tel: (+1) 805 446 4800 Fax: (+1) 805 446 4850	Kustermann-Park Balanstraße 59, D-81541 München Germany Tel: (+49) 894 549 490 Fax: (+49) 894 549 4949	7F, No. 50, Min Chuan Road Hsin-Tien Taipei, Taiwan Tel: (+886) 289 146 000 Fax: (+886) 289 146 639	Rm. 606, No.1158 Changning Road Shanghai, China Tel: (+86) 215 241 4882 Fax (+86) 215 241 4891	ANLIAN Plaza, #4018 Jintian Road Futian CBD, Shenzhen, China Tel: (+86) 755 882 849 88 Fax: (+86) 755 882 849 99	6 Floor, Changhwa B/D, 1005-5 Yeongtong-dong, Yeongtong-gu, Suwon-si, Gyeonggi-do, Korea 443-813 Tel: (+82) 312 731 884 Fax: (+82) 312 731 885