

An OLED bias supply for a clamshell handset sub display

Description

Portable applications such as cell phones are becoming increasingly complex with more and more features designed into every generation. One popular feature is to replace the STN sub display with an OLED sub display. OLED displays have infinite contrast ratio and are self-illuminating. This gives the handset manufacturer two key advantages, the first is lower power consumption and the second is a slimmer display. One disadvantage with OLED sub displays over LCD sub displays is the higher leakage current when not in use, which is the majority of the time. The way to overcome this issue is to disconnect the OLED sub display when the handset is dormant.

The ZXLB1600 is a boost converter that can provide the power requirements for OLED sub display with the additional feature of a fully integrated isolation switch which disconnects the input from output when the ZXLB1600 is shutdown, making it ideally suited to OLED biasing.

The schematic diagram in Figure 1 shows a full color OLED bias supply for clamshell handset sub display.

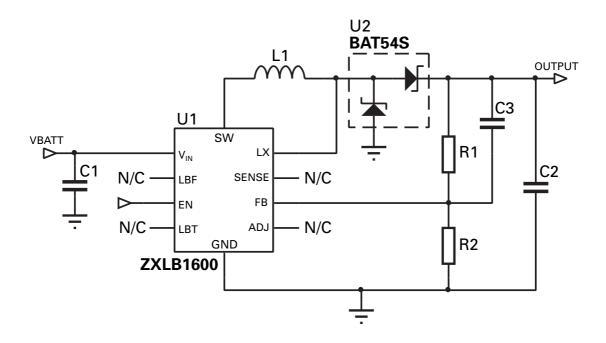


Figure 1 Schematic diagram

Note:

For applications where OLED leakage is not an issue and the ZXLB1600 isolation switch is not needed, the SW pin can be shorted to the V_{IN} pin, giving a further 3% to 5% improvement in efficiency.

The materials list and associated performance characteristics provide an OLED biasing solution for the following sub display specification:

• Input voltage: 4.2V to 3.0V

• Output voltage: 12V

• Output current: 20mA (max.)

• Output ripple: 50mVpk-pk (max.)

Reference	Value	Part number	Manufacturer	Contact details	Comments
U1		ZXLB1600X10	Zetex	www.zetex.com	OLED bias IC
U2		BAT54S	Zetex	www.zetex.com	Dual Schottky diode
L1	22μΗ	CMD4D11-220	Sumida	www.sumida.com	1mm height profile
R1	715kΩ	Generic	Generic	NA	0603 size
R2	82kΩ	Generic	Generic	NA	0603 size
C1	10μF/6V3	GRM series	Murata	www.murata.com	0805 size
C2 ⁽¹⁾	10μF/16V	GRM series	Murata	www.murata.com	1206 size
C3	82pF/16V	Generic	Generic	NA	0603 size

Table 1 Bill of materials

NOTES:

(1) For a lower profile, two $4.7\mu F$ 0805 capacitors can be used by connecting in parallel.

Typical operating characteristics

(For typical application circuit where V_{IN} = 3V, V_{OUT} = 12V, I_{OUT} = 20mA unless otherwise stated)



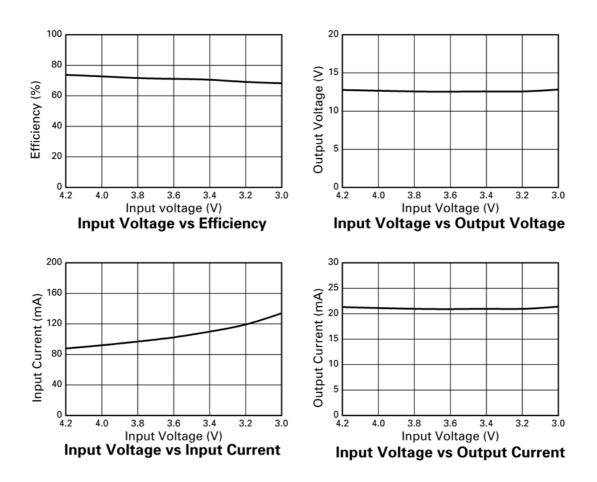


Figure 2 Performance graphs

Typical operating waveforms

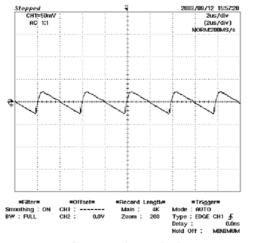
(For typical application circuit where V_{IN} = 3V, V_{OUT} = 12V, I_{OUT} = 20mA unless otherwise stated)



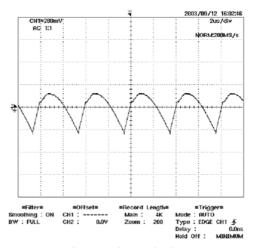

Output voltage ripple

Input voltage ripple

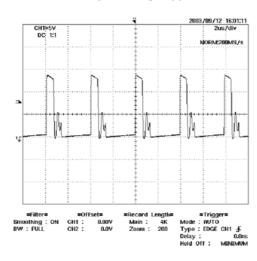

LX switching

Figure 3 Typical operating waveforms

Intentionally left blank

Americas Asia Pacific Corporate Headquarters Zetex GmbH Zetex Inc Zetex (Asia Ltd) Zetex Semiconductors plc Streitfeldstraße 19 700 Veterans Memorial Highway 3701-04 Metroplaza Tower 1 Zetex Technology Park, Chadderton D-81673 München Hauppauge, NY 11788 Hing Fong Road, Kwai Fong Oldham, OL9 9LL Germany Hong Kong United Kingdom Telefon: (49) 89 45 49 49 0 Telephone: (1) 631 360 2222 Telephone: (852) 26100 611 Telephone: (44) 161 622 4444 Fax: (49) 89 45 49 49 49 Fax: (1) 631 360 8222 Fax: (852) 24250 494 Fax: (44) 161 622 4446 europe.sales@zetex.com usa.sales@zetex.com asia.sales@zetex.com hq@zetex.com

For international sales offices visit www.zetex.com/offices

Zetex products are distributed worldwide. For details, see www.zetex.com/salesnetwork

This publication is issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contact or be regarded as a representation relating to the products or services concerned. The company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.