

Document DATE June 17, 2014		DOCUMENT-REV 1.0	PAGE Page 1 of 2
--------------------------------	--	------------------	---------------------


## PI6C557-03A Application and PCB Guide

Pericom Application Engineering

### 1. Introduction

PI6C557-03A is a high performance clock generator for PCIe 1.0 and 2.0 reference clock applications. This document is to provide customer application information.

### 2. Application Schematic

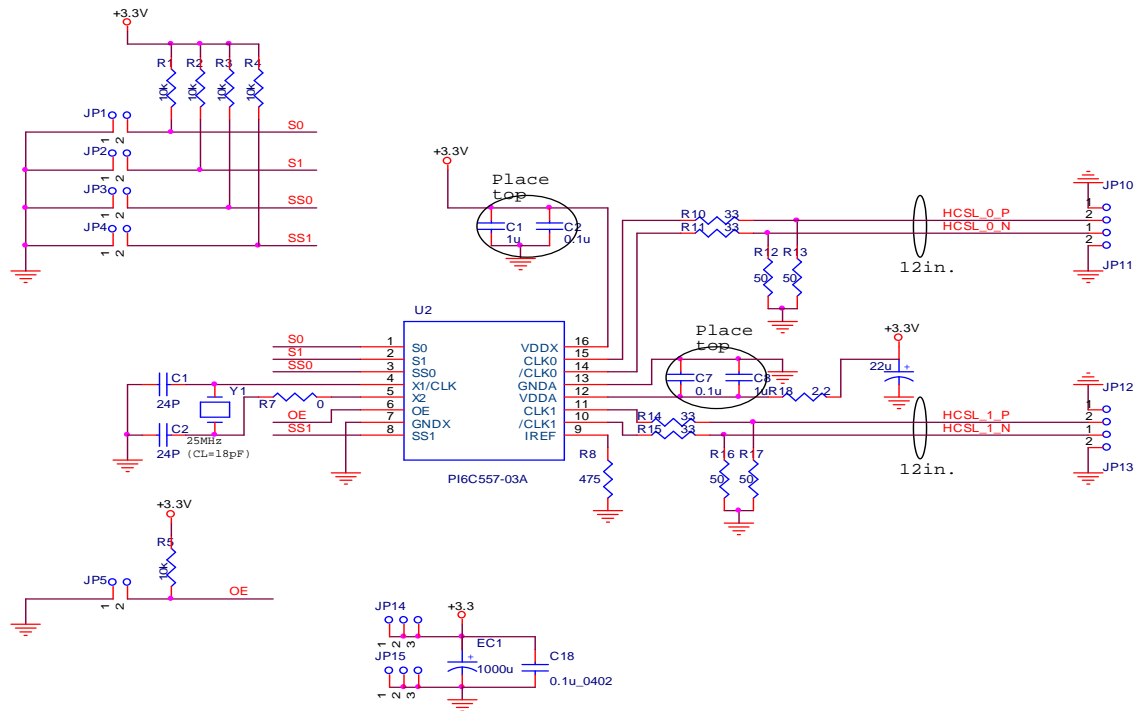

#### PCB Note:

- 1 Put each VDD 0.1uF decoupling cap. at least, all GND on one solid GND plane
- 2 On VDDA use serial 2.2 ohm in R7 to replace FB for better low frequency noise filtering
- 3 Leave un-used CLKx and /CLKx open
- 4 For small size crystal 3225 for example, choose R1=360
- 5 For output frequency and SSCG setting, please refer to the datasheet logic table

### 3. Crystal Circuit Layout

- 1) X1 and X2 pins are connected to crystal trace loop which should be very narrow without any board via in the loop and need keep-out around the traces;
- 2) Place crystal closer to the IC X1, X2 pins as possible and route crystal C1 and C2 load caps. on the top layer without via during to the crystal pins;
- 3) Keep external load cap. C4 and C5 GND pins close together to reduce board noise coupling into these caps. Design guide C1=C2=2x(CL-6) in -2pF if PCB trace has via, CL is any selected crystal's datasheet spec. load cap.


### 4. Crystal input (X1) CMOS Drive

X1 pin can accept external 25MHz CMOS input clock, just treat this X1 pin as general CMOS input pin, while leave X2 pin just simply open:

- (1) 3.3V 25MHz CMOS XO clock can directly in DC drive X1 pin;

Document DATE June 17, 2014		DOCUMENT-REV 1.0	PAGE Page 2 of 2
--------------------------------	--	------------------	---------------------

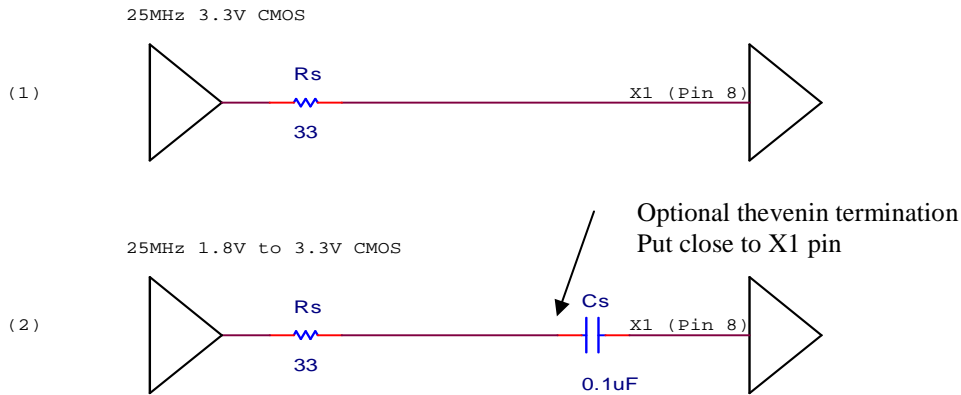- (2) For <3.3V 25MHz XO, it needs AC coupling to drive X1 pin.
- (3) The trace end pull-up/down in 100ohm thevenin termination is optional before drive X1 pin, which needs AC coupling too with V<sub>swing</sub> <3.3V. This way will consume bias current and more CMOS drive power.



External 25MHz XO Clock Drive X1 pin Example

### 5. HCSL Differential Output Layout

Place 33ohm serial and 50 ohm pull down <250mil close to IC output pins on comp. side. A 475 ohm resistor to GND must be connected on pin 9 (IREF) for output drive current control. PCB example is the following:

