

# AN45

## High voltage current monitoring using the ZXCT series in power supplies

by Peter Abiodun Bode, Snr. Applications Engineer

### Introduction

#### Power supply monitoring requirements

All power supplies and charging units have some current measurement requirement. The current levels measured will vary dependent upon the application. Operating input and required output voltage levels will differ in accordance with the system. For example, battery charger modules for PDA's can operate below 20V whilst measuring 1A to 2A, however a power supply for a bus converter will have very different requirements. A 700W power supply module will typically have current measuring requirements of tens of amps. By carefully setting the sense voltage to be used and determining the corresponding sense resistor,  $R_S$ , the ZXCT series in their basic form can cope with all of these.

Sometimes, it is necessary to monitor high side current circuits with operating voltages in excess of what the ZXCT series were designed for. The circuits outlined below demonstrate how a 20V current monitor can be used in applications with supply rails up to 250V and above.

#### High side high voltage current monitoring

One of the key benefits of the Zetex range of current-output current monitors (COCM's) is the very fact that their output is a current which, unlike their voltage-output (VOCM) counterpart, does not require an absolute ground reference to function. This means that the COCM device can be floated at a higher voltage and still ensure that its output current is available at a lower potential for translation to a ground-referenced output voltage.

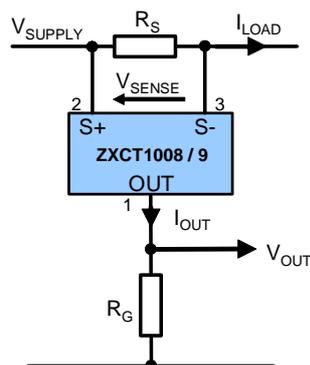


Figure 1 Simplest 3-terminal COCM


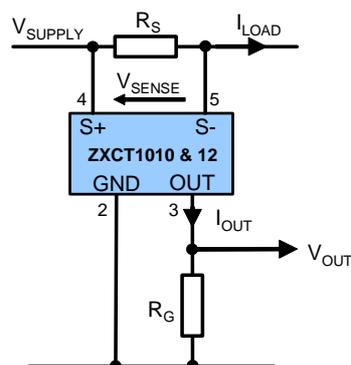



Figure 2 Simplest 4-terminal COCM

Figure 1 and Figure 2 show the basic configuration of 3- and 4-terminal current-output current monitors. In this form, the maximum operating voltage will be limited to that of the COCM itself (typically 20V, 40V or 60V). However, with the addition of only one or three components, the range of operation can be extended to much higher voltages. The methods for achieving this are illustrated in Figure 3, Figure 4 and Figure 5


# AN45

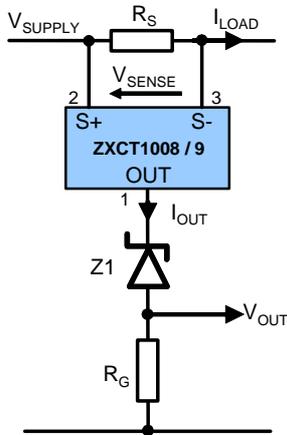

**Figure 3 Simplest supply range extension**

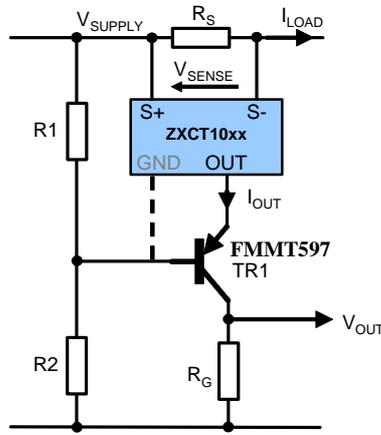

**Figure 4 Improved supply range extension**

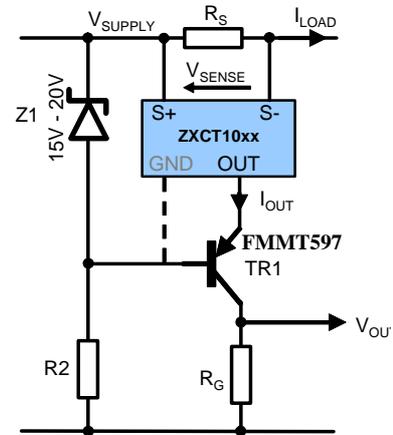

**Figure 5 Best supply range extension**

Suitable devices: All COCM's

## Circuit explanation

The three circuits are discussed in detail below.

### High voltage Option 1

Figure 3 is the simplest to use if the supply voltage is essentially fixed and does not vary much and satisfies the following criteria,

$$\Delta V_{SUPPLY} \leq V_{MAX} - V_{DO} \quad \text{Equation 1}$$

$$V_{SUPPLY(min)} \geq V_{DO} + V_{OUT(max)} + V_Z \quad \text{Equation 2}$$

$$V_{SUPPLY(max)} \leq V_{WM} + V_Z \quad \text{Equation 3}$$

where,

$V_Z$  = Zener operating voltage

$V_{MAX}$  = Maximum operating voltage (20V in most cases)

$V_{SUPPLY(min)}$  = Minimum supply operating voltage,

$V_{SUPPLY(max)}$  = Maximum supply operating voltage,

$V_{DO}$  = Drop-out voltage (absolute minimum voltage across device, S+ & OUT pins)

It can only be used with a 3-terminal COCM. If the supply varies too much and/or it is required to use a 4-terminal COCM, either Figure 4 or Figure 5 will have to be used.

Besides the limitations in Equation 1 and Equation 2, the only other limitation on this method is the power dissipation in the zener diode.

**Design Example 1**

It is required to measure the load current of a 100V power supply which delivers 5A into the load. The supply's tolerance is stated at  $\pm 5\%$ . The output voltage needs to be scaled to 5V at full load.

**Solution**

The minimum to maximum supply range is 95V to 105 representing a change of 10V. This change is well within the operating range of the ZXCT1009 of 2.5V to 20V and meets the requirements of Equation 1. Therefore use the option in Figure 3.

Transposing Equation 1 above,

$$\begin{aligned} V_Z &\leq V_{SUPPLY(\min)} - (V_{DO} + V_{OUT(\max)}) && \text{Equation 4} \\ V_Z &\leq 87.5V \end{aligned}$$

Transposing Equation 2 above,

$$\begin{aligned} V_Z &\geq V_{SUPPLY(\max)} - V_{WM} && \text{Equation 5} \\ V_Z &\geq 85V \end{aligned}$$

Hence, the zener diode's voltage rating needs to be between 85V and 87.5V. If the range of zener voltage does not cover common standard values, as in this case, the required voltage could be made up with two zener diodes in series. For example it is possible to use two 43V zeners in series to form an 86V zener diode.

The next parameter to check is to make sure that the zener diode(s) dissipation is taken into consideration. For this it is necessary to know what  $I_{OUT}$  is. This can be approached in one of two ways, either from the input to the output or, from the output to the input depending on which parameter there is greater control of. If optimum accuracy is paramount and it is possible to have full control of the choice of zener dissipation, work from the input. If zener dissipation is a given, then work from the output. In either case the set of equations required are the same except that they need to be worked iteratively to make sure they are not breaking any of the design parameters.

So, assume that a zener diode rated at 300mW. As a general rule, it is necessary to apply a derating factor to this, for example 50%. Hence  $I_{OUT}$  is given by:

$$I_{OUT} = \frac{P_Z}{V_Z} \cdot 0.5 = \frac{0.3 \cdot 0.5}{86} = 1.74mA \quad \text{Equation 6}$$

Since  $V_{OUT}$  is known,  $R_G$  can now be determined, but it is wise to determine  $R_S$  first in case of the need to adjust  $I_{OUT}$  to take into consideration the range limitations of  $V_{SENSE}$ , power dissipation in  $R_S$  and the limited choice of  $R_S$  values. There is far more freedom in choosing  $R_G$  than in  $R_S$  which is typically less than 1 Ohm.

Check for sensible values of  $R_S$  and  $V_{SENSE}$  to obtain an output current of around 1.74mA.

$$V_{SENSE} = \frac{I_{OUT}}{G_T} = \frac{1.74}{0.01} = 174mV$$

# AN45

Which will require an  $R_S$  value of

$$R_S = \frac{V_{SENSE}}{I_{LOAD}} = \frac{0.174}{5} = 34.8m\Omega$$

It is unlikely to find a  $34.8m\Omega$  resistor so it is necessary to choose the nearest standard value.  $33m\Omega$ , a value within the E12 value series, is more likely and represents only -5% deviation from the calculated value (remember the zener power is derated by 50%, so there is plenty of margin).

Using this value, the true values of  $V_{SENSE}$  and  $I_{OUT}$  will be

$$V_{SENSE} = R_S \cdot 5 = 0.033 \cdot 5 = 165mV$$

$$I_{OUT} = G_T \cdot V_{SENSE} = 0.01 \cdot 0.165 = 1.65mA$$

which is even less than the original estimate, so it is known to be within acceptable limits.

Finally  $R_G$  can be determined by,

$$R_G = \frac{V_{OUT}}{I_{OUT}} = \frac{5}{1.65} = 3.03k\Omega$$

So, use a  $3k\Omega$  resistor for a cumulative error of 1%, or determine if  $3.03k\Omega$  can be found in higher electrical (E) series, or make up this value with a series or parallel resistor combination. For example  $3k$  in series with  $30\Omega$  or  $3k3$  in parallel with  $36k$  or  $39k$ .

The solution of the problem is shown below in Figure 6.

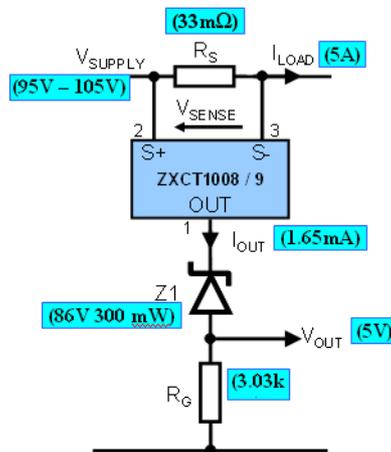


Figure 6 Solution to Design Example 1

## High voltage Option 2

The previous example in Figure 3 has a very limited supply variation range. Figure 4 is a little more flexible as it dynamically varies the voltage drop across both  $R_1$  and  $R_2$  to compensate for varying supply voltage.

TR1 is used in the common base configuration and is used to drop most of the supply voltage between collector and emitter. When the current gain is reasonably high ( $>100$ ),  $I_C \approx I_E$  and  $I_{OUT}$  still flows through  $R_G$  and hence  $V_{OUT}$  can still be calculated in the normal way.

Ideally, R1 must be chosen to keep within the ZXCT's normal supply range, large enough in value to provide the minimum operating voltage to the device at the lowest supply voltage but not too large that the maximum device operating voltage is exceeded at the highest input voltage.

#### Procedure 1 - Design steps for Figure 4

1. Determine or estimate  $I_{OUT}$  (it doesn't need to be precise at this stage)
2. Determine the required minimum supply voltage,  $V_{SUPPLY(min)}$ .
3. Determine device's maximum working voltage,  $V_{MAX}$ .
4. Calculate transistor bias current  $I_B$  from  $I_B = \frac{I_{OUT}}{h_{FE(min)}}$

5. Calculate bias resistor RB from

$$R_B = \frac{(V_{SUPPLY(min)} - V_{DO} - V_{eb})}{I_B} = \frac{(V_{SUPPLY(min)} - V_{DO} - V_{eb}) \cdot h_{FE(min)}}{I_{OUT}} = \frac{R1 \cdot R2}{R1 + R2}$$

6. Calculate R1 from  $R1 = \left( \frac{V_{SUPPLY(max)}}{V_{SUPPLY(max)} - V_{MAX}} \right) \cdot R_B$

7. Calculate R2 from  $R2 = \left( \frac{V_{SUPPLY(max)}}{V_{MAX}} \right) \cdot R_B$

#### High voltage Option 3

In a situation where a higher supply voltage is required or where the supply voltage varies over a wide range, the scheme in Figure 5 could be used where resistor R1 in Figure 4 is replaced with a zener diode rated within the maximum working voltage of the COCM. The design steps are similar to those in Procedure 1 but slightly simpler.

#### Procedure 2- Design steps for Figure 5

1. Determine or estimate  $I_{OUT}$  (it doesn't need to be precise at this stage)
2. Determine device's maximum working voltage,  $V_{MAX}$ .
3. Chose the value of Z1 to be within  $V_{MAX}$  e.g.  $V_Z=15V$  for a  $20V_{MAX}$  device.  
In general, make sure  $(V_{DO} + V_{be}) < V_Z \leq V_{MAX}$
4. Determine the required minimum supply voltage,  $V_{SUPPLY(min)}$ .
5. Compute transistor bias current  $I_B$  from  $I_B = \frac{I_{OUT}}{h_{FE(min)}}$
6. Compute resistor R2 from


$$R2 = \frac{(V_{SUPPLY(min)} - V_Z)}{I_B} = \frac{(V_{SUPPLY(min)} - V_Z) \cdot h_{FE(min)}}{I_{OUT}}$$

# AN45


## High voltage Option 4

Both Options 2 and 3 (Figure 4 and Figure 5) provide wider range operation than is possible with Figure 3. However neither would be suitable for devices such as ZXCT1050 whose common mode range include ground. What is required is a scheme that extends the supply voltage (or common mode) range but does not at the same time raise it from ground. Figure 7 below shows how this can be done.

A resistor, R3, is connected from the S- pin to ground so as to form a potential divider with the transconductance resistor, R<sub>GT</sub>. The S+ pin is similarly connected to another potential divider formed by R1, R2. It must be ensured that the ratios (not the absolute values) of the two potential dividers are exact. In other words, R1/R2 must be equal to R<sub>GT</sub>/R3. Failure to observe this rule will result in massive common mode error that would render the scheme practically useless. In addition, the resistors themselves need to be very closely matched to much better than 1%.

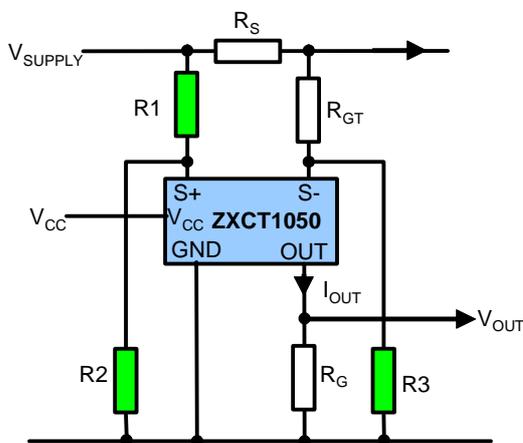

**Figure 7** Extending the CM range of the ZXCT1050 (using precision resistors)

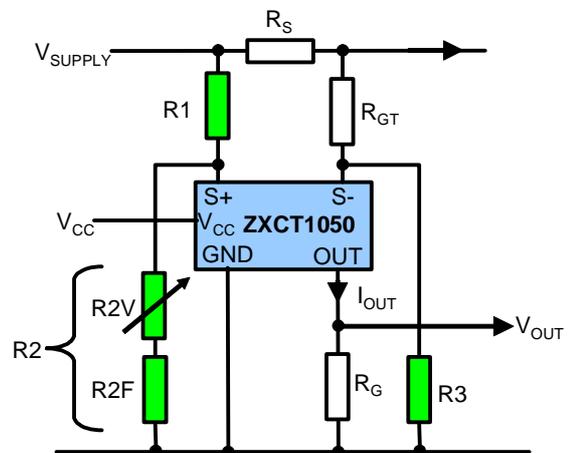

**Figure 8** Using non-precision resistors to extend CM range (using standard resistors)

Hence, one resistor could be replaced by a trimmable resistor to balance both legs. This way, less than precise values could be used to start with as shown in Figure 8. Here, R2 has been replaced by the combination of a fixed and a variable resistor<sup>1</sup>. Now, the resistors do not have to be low tolerance ones and standard 1% or even 2% resistors can be used. What is more important is stability. So, in any case, always make sure that high stability resistors are used. Metal film resistors are generally very good for this.

### Procedure 3- Design steps for extending CM range and Figure 7 and Figure 8

1. Determine the maximum required supply voltage,  $V_{S(max)}$ .

2. Calculate R3 from 
$$R3 = \frac{R_{GT}}{\left(\frac{V_{S(max)}}{V_{CC} - 2}\right) - 1}$$

3. Make R3 the nearest lower preferred value. E.g. if the result of 2 above were 69.35k, then choose 68k as the nearest lower preferred value.

4. Next, determine R1 and R2 from  $\frac{R1}{R2} = \frac{R_{GT}}{R3}$ . The easiest thing to do is to simply make

$R1=R_{GT}$  and  $R2=R3$ . It's possible to make  $R1=nR_{GT}$  and  $R2=nR3$  where  $n$  is any arbitrary number, preferably not less than 1. The advantage of making  $n$  greater than 1 is that the current down the potential divider network formed by R1, R2 can be kept to a minimum. Be careful however not to make  $n$  too high as it then begins to introduce offset errors into the circuit. A value of  $n$  between 1 and 10 is quite reasonable.

<sup>1</sup>Note that it is not recommended to make all of R2 variable as this would result in very low resolution, increased potential for long term drift and make the circuit more susceptible to thermal and mechanical shock effects.

This is all that is required as far as using high precision resistors is concerned (Figure 7). In order to use standard resistors however (Figure 8) the following steps are required as well.

5. Determine the tolerance, Tol, of resistors being used, e.g. 1%.
6. Calculate R2V from  $R2V \geq \frac{8 \cdot Tol}{100} \cdot R2$  and select the nearest higher preferred value.
7. Calculate R2F from  $R2F \leq \left(1 - \frac{4 \cdot Tol}{100}\right) \cdot R2$  and select the nearest lower preferred value.

Make sure that R2V is a good quality variable resistor (e.g. cermet type). If the circuit is going to be subjected to a wide temperature range, it would also be advisable to make sure that the temperature coefficient of R2V is comparable to that of the fixed resistors.

## Conclusion

Current output current monitors have a limited voltage range. However, use of a few extra components allows their voltage capability to be extended to hundreds of volts. Several techniques have been discussed which shows the flexibility and usefulness of current output current monitors.

## Recommended further reading

1. AN39 - Current Measurement Applications Handbook
2. DN77 - Transient and noise protection for current monitors

# AN45

---

## Definitions

### Product change

Zetex Semiconductors reserves the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

### Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Zetex with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Zetex does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

### Life support

Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Zetex Semiconductors plc. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

### Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

### Terms and Conditions

All products are sold subjects to Zetex' terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Zetex sales office .

### Quality of product

Zetex is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Zetex Semiconductors or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: [www.zetex.com/salesnetwork](http://www.zetex.com/salesnetwork)

Zetex Semiconductors does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

### ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

### Green compliance

Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

### Product status key:

|                                   |  |
|-----------------------------------|--|
| "Preview"                         | Future device intended for production at some point. Samples may be available  |
| "Active"                          | Product status recommended for new designs                                     |
| "Last time buy (LTB)"             | Device will be discontinued and last time buy period and delivery is in effect |
| "Not recommended for new designs" | Device is still in production to support existing designs and production       |
| "Obsolete"                        | Production has been discontinued   |

### Datasheet status key:

|                       |   |
|-----------------------|---|
| "Draft version"       | This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.  |
| "Provisional version" | This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice. |
| "Issue"               | This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.  |

### Zetex sales offices

#### Europe

Zetex GmbH  
Kustermann-park  
Balanstraße 59  
D-81541 München  
Germany  
Telephone: (49) 89 45 49 49 0  
Fax: (49) 89 45 49 49 49  
europe.sales@zetex.com

#### Americas

Zetex Inc  
700 Veterans Memorial Highway  
Hauppauge, NY 11788  
USA  
Telephone: (1) 631 360 2222  
Fax: (1) 631 360 8222  
usa.sales@zetex.com

#### Asia Pacific

Zetex (Asia Ltd)  
3701-04 Metroplaza Tower 1  
Hing Fong Road, Kwai Fong  
Hong Kong  
Telephone: (852) 26100 611  
Fax: (852) 24250 494  
asia.sales@zetex.com

#### Corporate Headquarters

Zetex Semiconductors plc  
Zetex Technology Park, Chadderton  
Oldham, OL9 9LL  
United Kingdom  
Telephone: (44) 161 622 4444  
Fax: (44) 161 622 4446  
hq@zetex.com

---

© 2007 Published by Zetex Semiconductors plc