

#### **General Description**

Based on Flyback topology, the Primary side Regulated AP3781 EV board is designed to serve as an example for High Efficiency, low cost & less components for consumer home appliance and power tools system. This system output is 70W with 23V-3A. It can meet DOE VI and CoC Tier 2 energy efficiency requirement.

#### **Key Features**

- 90 ~264V<sub>AC</sub> wide input range
- Use the Primary side control to eliminate the Opto-coupler.
- PFM method operations.
- With Valley on detection, the switching stays at Valley. So that will realize good system efficiency & EMI performance, and above 90% efficiency can be reached at full load.
- Low start-up operating quiescent currents, 150mW low standby input power can be achieved.
- Accurate constant voltage (CV)& constant current (CC) regulation performance.
- Good EMI performance with IC Jittering Frequency function
- Internal Auto Recovery OCP, OVP, OLP, OTP Power Protection, cycle by cycle current limit.
- Adjustable cable Compensation.
- With a Brown out Protection.

#### **Applications**

- Switching AC-DC Adaptor & Charger
- Home Appliances systems
- Power Tools
- Battery charger

Universal AC input PSR 23V-3.0A Power Specifications (CV & CC mode)

Parameter	Value
Input Voltage	90 to 264V <sub>AC</sub>
Input standby power	150mW
Main output Vo / Io	23V – 3A
Efficiency	~ 90%
Total Output Power	70W
Protections	OCP, OVP, OLP,OTP
XYZ Dimension	84 x 53 x 20 mm
ROHS Compliance	Yes

#### **Evaluation Board Picture:**

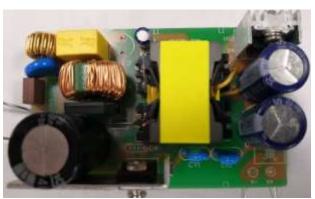
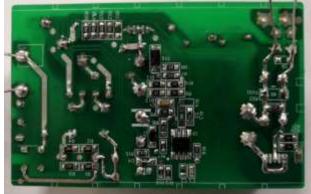


Figure 1: Top View

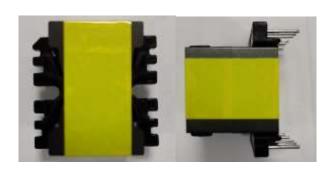


**Figure 2: Bottom View** 




AP3781 (90 V<sub>AC</sub> ~ 265 V<sub>AC</sub> one outputs 70W Transformer Spec.)

## 1) Core & Bobbin: PQ26/20, 5+2 pin



## 2) Electrical Diagram:

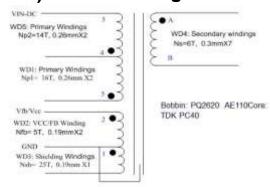

# 3) Transformer Parameters

1. Primary Inductance (Pin5-Pin3), all other windings are open Lp =0.35 mH ±7% @10KHz

PQ2620	PQ2620 (Ae = 110mm^2)						
NO NO		TERMINAL NO.		WINDING			
Winding	NAME	START	FINISH	WIRE	TURNS	Layers	
1	Np1	5	4	Φ 0.26mm X 2	16 Ts	2	
2	Na	2	1	Φ 0.19mm X 2	5 Ts	2	
3	Ns	A	В	Φ 0.30mm X 7 6 Ts		2	
4	Shield	1 (GND)	NC	Φ 0.19mm X 1	25 Ts	2	
5	Np2	4	3	Φ 0.26mm X 2	14 Ts	2	
Primary In	ductance	Pin 5-3,all other windings open, measured at 10kHz, 0.4VRMS			0.35mH ±	7 %	
Primary Lo Inductance	•	Pin 5-3, all other windings shorted, measured at 10kHz, 0.4VRMS			25 uH (Ma	x.)	

### **Evaluation Board Schematic**

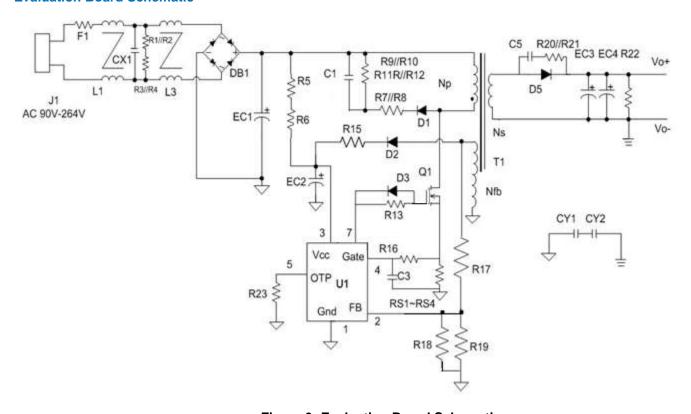


Figure 3: Evaluation Board Schematic

#### **Evaluation Board PCB Layout**

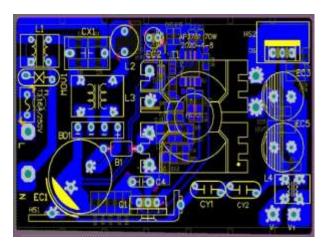


Figure4: PCB Board Layout Top View

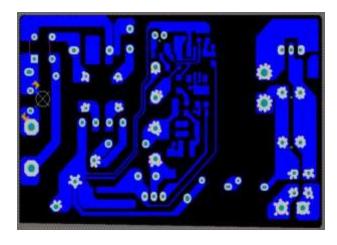


Figure 5: PCB Board Layout Bottom View



### **PCB Layout Consideration**

As shown in Figure 6, there are four major high frequency current loops:

- 1. The current path from bulk capacitor, transformer, MOSFET, Rcs returning to bulk capacitor
- 2. The path from GATE pin, MOSFET, Rcs returning to the ground of IC
- 3. The RCD clamp circuit is a high frequency loop
- 4. Transformer, rectifier diode, and output capacitor also a high frequency current loop

The loops must be as short as possible to decrease the radiate area for a better EMI, and if the MOSFET And Schottky diode have heat sink, the heat sink should be connected to their ground separately.

### **Ground Layout Consideration**

- 1. A proper "Ground" layout is important to decrease unknown noise interference and EMI issue in the switching power supply.
- 2. A so-called "Star" connection is highly recommended for primary GND. As shown in Figure 6, the ground of MOSFET, auxiliary winding, Y-cap and control IC are separated and finally connected together on bulk capacitor ground. The width of these grounds should be kept as large as possible. The primary side of Y-cap could also be connected to the high voltage pin

### **Evaluation Board PCB Layout**

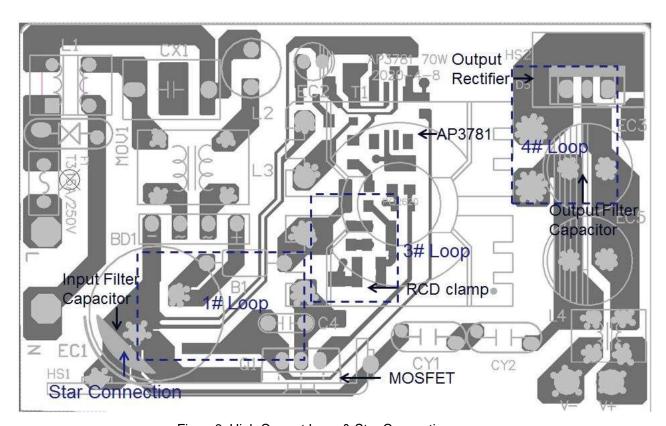


Figure6: High Current Loop & Star Connection



#### **Quick Start Guide**

- 1. The evaluation board is preset at 23V/3A from output + & -
- 2. Ensure that the AC source is switched OFF or disconnected before doing connection.
- 3. Connect the AC line wires of power supply to "L and N" on the left side of the board.
- 4. Turn on the AC main switch.
- 5. Measure Red & Black wires to ensure correct output voltages at 23V respectively.

#### **Build of Material**

			AP3781 23V-3A BOM 6-5-2020		
Item	QTY per board	REF. DES.	Description	MFG or Supplier	MFG P/N or Supplier P/N Digi key #
1	1	EC1	120uf /400V 16 x 32mm	Aishi Electro	
2	1	EC2	10uF/50V 5 x 10mm	Aishi Electro	
3	2	EC3, EC4	1000uf /35V 12 x 16mm	Aishi Electro	
4	1	C1	1nf / 1KV, 1206 X7R	Holy Stone	
5	1	C3	33pf / 25V, 0805 X7R	Holy Stone	
6	1	C5	1nf / 200V, 0805 X7R	Holy Stone	
7	4	R1,R2,R3,R4	2M ohm 1206	Yageo	
8	2	R5,R6	1M ohm 1206	Yageo	
9	2	R7,R8	51R ohm 1206	Yageo	
10	4	R9,R10,R11,R12	180K ohm 1206	Yageo	
11	1	R13	20R ohm 1206	Yageo	
12	1	R15	1R ohm 0805	Yageo	
13	1	R16	1K ohm 0805	Yageo	
14	1	R17	47.5K ohm 0805	Yageo	
15	1	R18	7.5K ohm 0805	Yageo	
16	1	R19	82.5K ohm 0805	Yageo	
17	4	RS1,RS2.RS3,RS4	1.0R ohm 1206	Yageo	
18	2	R20,R21	10R ohm 1206	Yageo	
19	1	R22	12K ohm 1206	Yageo	
20	1	BD1	KBP410G	Diodes	
21	1	D1	S2MA SMA	Diodes	
22	1	D2	RS1MSWF SOD-123	Diodes	
23	1	D5	SDT40A120CT	Diodes	
24	1	F1	3.15A330V	Fuse	
25	1	L1	1mH 8X10mm	Inductor	
26	1	L2	20mH 10X20mm	Inductor	
27	2	CY1,CY2	3.3nf/250Vac Y1	Holy Stone	
28	1	U1	AP3781 sop-7	Diodes	
29	1	Q1	250N65S3	ONsemi	
30	1	T1	PQ26/20		

AP3781 23V-3A BOM 6-5-2020

Notes: 1. D2 diode type selection, we propose standard or fast diode (not schottky or super fast recovery diode).

**Input Standby Power** 

Input Voltage	115Vac/60Hz	230Vac/50Hz	Note
Pin (w) 90mW		140mW	At no loading


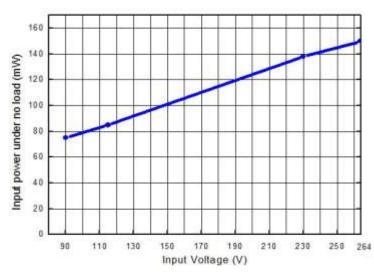


Figure 8: The Efficiency curve with at different AC input

## Input power Efficiency at different loading

AC input	Efficiency (%)					Eff_avg at four
AC Iliput	10%	25%	50%	75%	100%	conditions
115VAC/60Hz	89.49%	90.84%	90.61%	90.49%	90.09%	90.50%
230VAC/50Hz	88.22%	91.20%	91.80%	91.89%	91.96%	91.71%
Eff_avg						

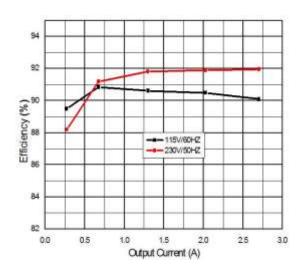

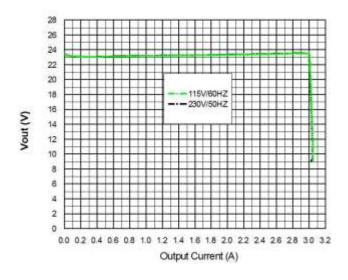




Figure 9: The efficiency curve with different loading

Figure 10: CV & CC Curve at OCP set poits

# **OCP Current set point with at different AC line**

AC input	90VAC	115VAC	230VAC	264VAC	Note
I _max	3A	3A	3A	3A	

# **PSU Output Characteristics:**

### Line Regulation (at full loading condition):

AC input Voltage	90Vac/60Hz	115VAC/60Hz	230Vac/50Hz	265VAC/50Hz	Note
23.00Vout	23.43V/2.7A	23.47V/2.7A	23.51V/2.7A	23.51V/2.7A	0.34%<1%

### **Cross Load Regulation (at nominal line AC input voltage):**

AC input Voltage	115VAC/60Hz	230VAC/50Hz
23V Full Load	23.46V / 2.7A	23.50V/2.7A
23V 10% of FL	23.04V /0.27A	23.05V/0.27A
Note: cable compensation	1.82%	1.95%

Note: All output voltages are measured at output PCB board Edge. Internal Cable Compensation 4%

# **Key Performance Waveforms:**

### System start - up time

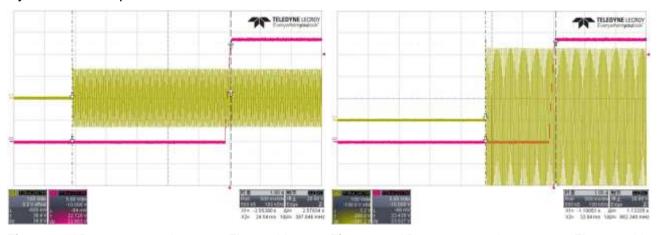


Figure 11:AP3781 turn on time 2.57sFL at 90Vac

Figure 12: AP3781 turn on time 1.13s at FL, at 230Vac

# System main switching Voltage Stress on Q1 D-S

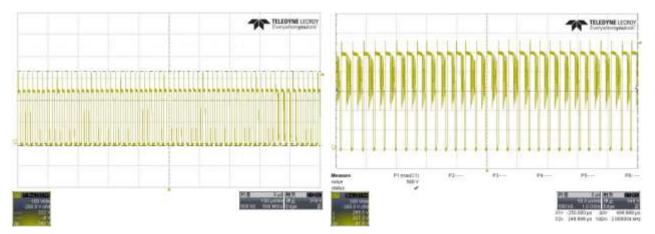


Figure 13:AP3781 Vds at FL at 90Vac Vds=340Vp-p Figure 14: AP3781Vds at FL at 264Vac, Vds=566Vp-p

# System Voltage Stress across on D5 A-C

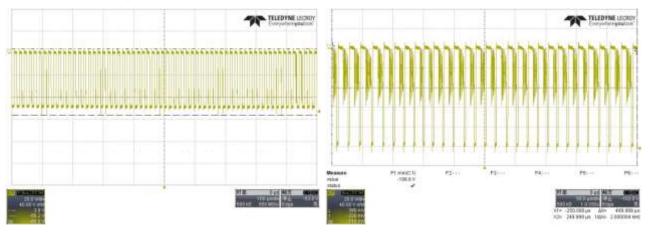


Figure 15: D5 A-C voltage stress at 90Vac FL Vd = 60Vp-p 20V/div

**Figure 16:** D5 A-C voltage stress at 264Vac at FL Vd = 106.6Vp-p 20V/div



### System output Ripple performance

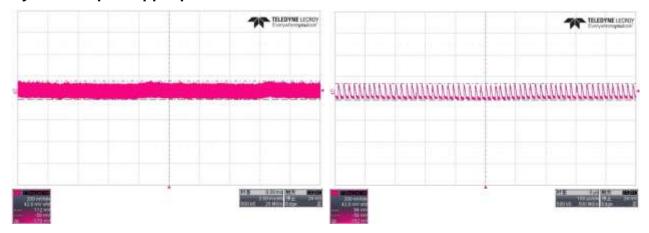


Figure 17: The Ripple at 115Vac\_in Vpp=170mv FL Figure 18: The Ripple at 230Vac\_in Vpp=160mv FL System Dynamic Response performance

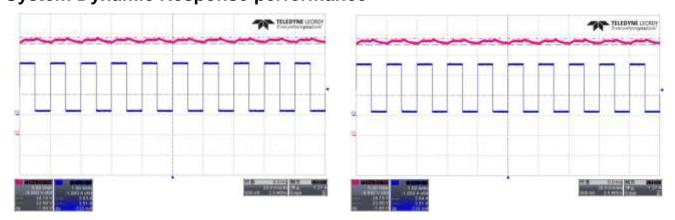


Figure19:115VAC; Load level: 0.27~2.7A; Vout:22.5~24.1V Figure20: 230VAC; Loadlevel:0.27~2.7A; Vout: 22.5~24.1V Frequency: 10ms~10mS. Slew rate: 0.25A/us Frequency: 10ms~10mS. Slew rate: 0.25A/us

AP3781 EV1 Page 9 of 14 06 -05. 2020 Rev1.0 www.diodes.com

## **System Dynamic Response performance**


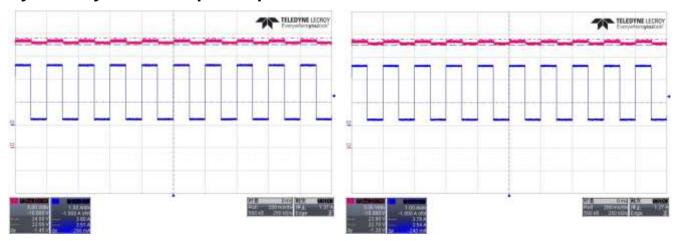


Figure 21: 115VAC; Load level: 0.27~2.7A; Vout:22.5~24.0V Figure 22: 230VAC; Load level: 0.27~2.7A; Vout:22.7~23.9V Frequency: 100ms~100mS. Slew rate: 0.25A/us Frequency: 100ms~100mS. Slew rate: 0.25A/u

# Thermal Test data at room Temperature after running 1 hr

90Vac full load

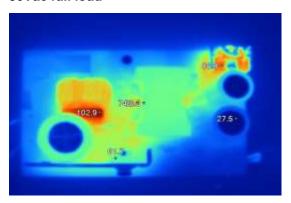


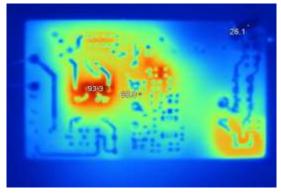


Figure 23 Ta 27.5°C DB1 KBP410 102.9°C Q1 250N65 61.7°C T1 74°C D5 40A120 86.8°C **264Vac full load** 

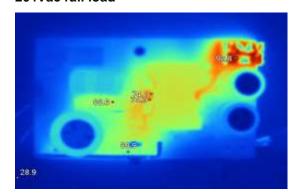

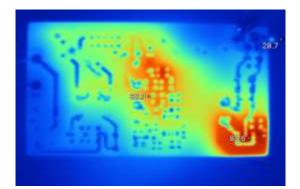


Figure 24 Ta 28°C, DB1 KBP410 66.6°C Q1 250N65 60.9°C T1 74.2°C D5 40A120 92.8°C



## System EMI L-Line Scan Data(at 115Vac)

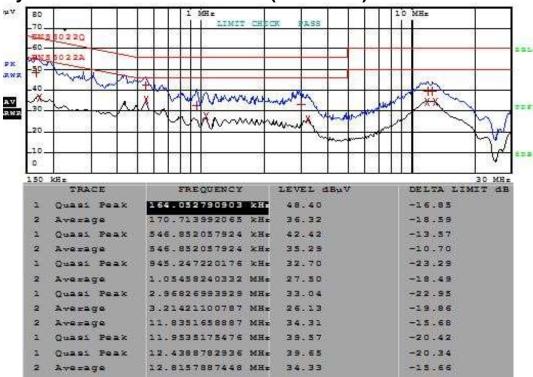


Figure 25: EMI Scan at 115Vac

## System EMI N-Line Scan Data(at 115Vac)

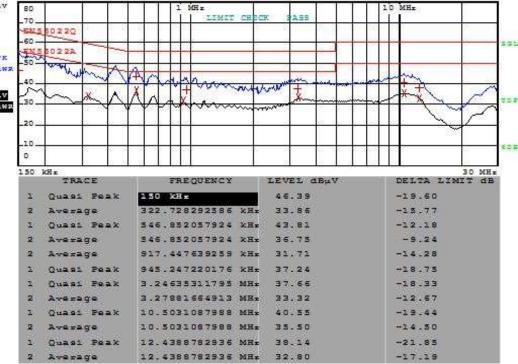


Figure 26: EMI Scan at 115Vac



## System EMI L-Line Scan Data(at 230Vac)

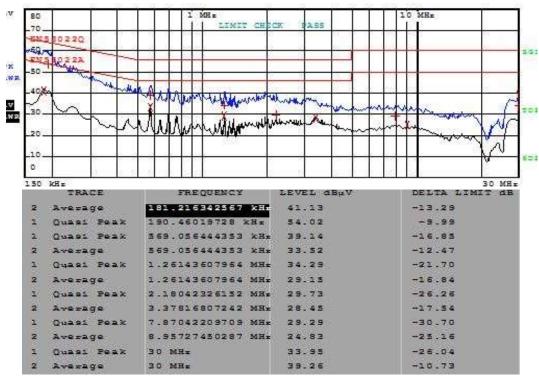


Figure 27: EMI Scan at 230Vac

## System EMI N-Line Scan Data(at 230Vac)

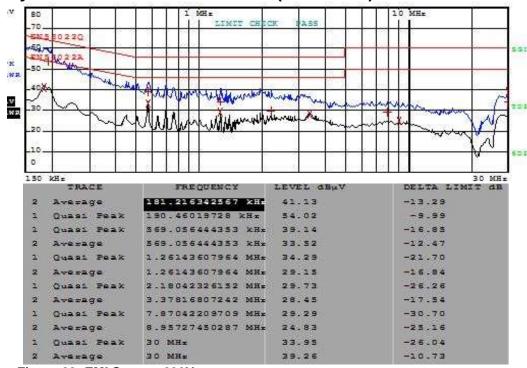


Figure 28: EMI Scan at 230Vac



Please see the recommand Application note for reference (web page - http://www.diodes.com/appnote\_dnote.html)



#### IMPORTANT NOTICE

DIODES INCORPORATED MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARDS TO THIS DOCUMENT, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION).

Diodes Incorporated and its subsidiaries reserve the right to make modifications, enhancements, improvements, corrections or other changes without further notice to this document and any product described herein. Diodes Incorporated does not assume any liability arising out of the application or use of this document or any product described herein; neither does Diodes Incorporated convey any license under its patent or trademark rights, nor the rights of others. Any Customer or user of this document or products described herein in such applications shall assume all risks of such use and will agree to hold Diodes Incorporated and all the companies whose products are represented on Diodes Incorporated website, harmless against all damages.

Diodes Incorporated does not warrant or accept any liability whatsoever in respect of any products purchased through unauthorized sales channel.

Should Customers purchase or use Diodes Incorporated products for any unintended or unauthorized application, Customers shall indemnify and hold Diodes Incorporated and its representatives harmless against all claims, damages, expenses, and attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized application.

Products described herein may be covered by one or more United States, international or foreign patents pending. Product names and markings noted herein may also be covered by one or more United States, international or foreign trademarks.

This document is written in English but may be translated into multiple languages for reference. Only the English version of this document is the final and determinative format released by Diodes Incorporated.

#### **LIFE SUPPORT**

Diodes Incorporated products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Diodes Incorporated. As used herein:

- A. Life support devices or systems are devices or systems which:
  - 1. are intended to implant into the body, or
  - 2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in significant injury to the user.
- B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Customers represent that they have all necessary expertise in the safety and regulatory ramifications of their life support devices or systems, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of Diodes Incorporated products in such safety-critical, life support devices or systems, notwithstanding any devices- or systems-related information or support that may be provided by Diodes Incorporated. Further, Customers must fully indemnify Diodes Incorporated and its representatives against any damages arising out of the use of Diodes Incorporated products in such safety-critical, life support devices or systems.

Copyright © 2016, Diodes Incorporated

www.diodes.com